

Answers


Electronics revision questions

1. input process output

2. a) digital
b) analogue
c) digital
d) digital
e) analogue

3. a--- digital
b--- analogue
c--- analogue
d --- analogue
e --- digital

4. thermistor

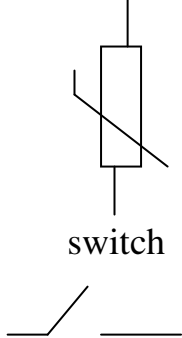

switch


thermocouple



microphone




capacitor

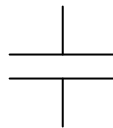


potentiometer



LDR

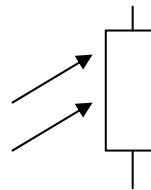

solar cell

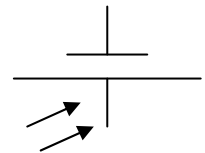

5. a) thermistor ---- analogue
b) thermocouple ---analogue
c) capacitor -----analogue
d) LDR --- analogue
e) solar cell --- analogue
f) switch --- digital
g) microphone ---analogue
h) potentiometer --- analogue

6. a) thermistor ---- electronic thermometer
- b) thermocouple --- electronic thermometer- high temperature
- c) capacitor -----time delay in a burglar alarm
- d) LDR --- light meter sensor
- e) solar cell --- charger unit in a calculator
- f) switch --- door sensor in burglar alarm
- g) microphone --- public address system
- h) potentiometer --- speed control on a toy car

7. resistance decreases


8. resistance decreases


9. 500Ω

10. increases resistance or increase capacitance


11. voltage divider

12. 1.52V

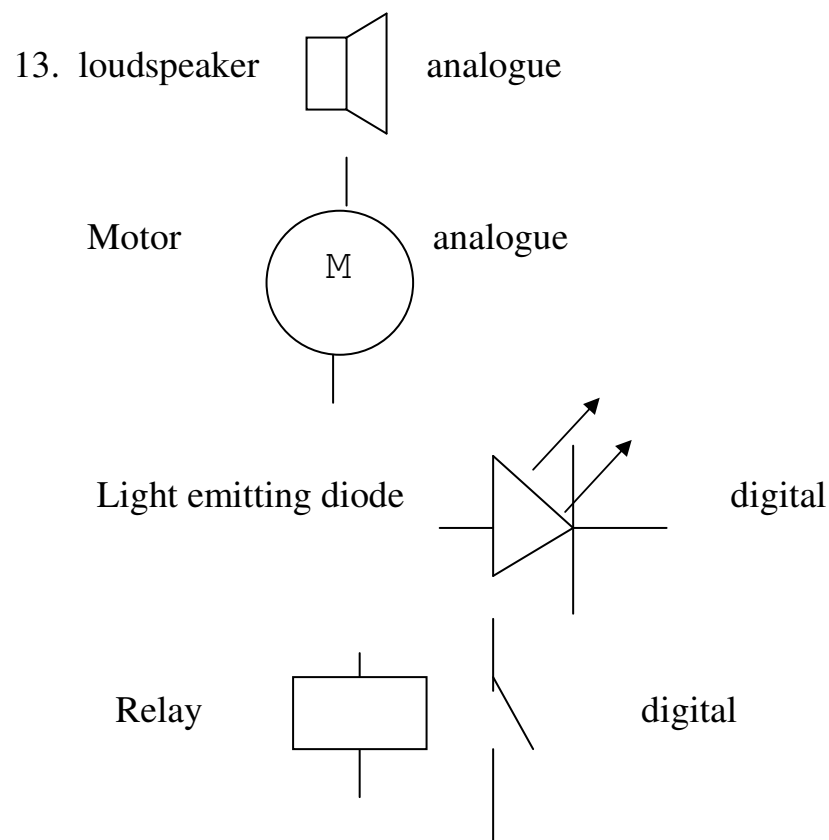

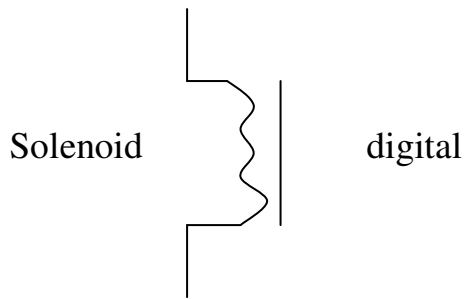

Seven segment display

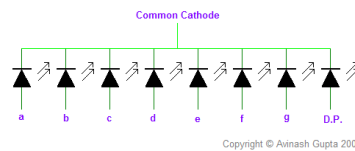

digital

14. It will only conduct current in one direction.

15. To stop too much current flowing through it and damaging it.

16. 0 -- abcfed

1 -- bc

2 -- abged

3 -- abcdg

4 -- fgbc

5 -- afgcd

6 -- afedcg

7 -- abc

8 -- abcdefg

9 -- abcdgf

17. a) *loudspeaker*

b) *7 segment display*


c) *LED*

d) *relay*

e) *solenoid*

f) *motor*


18.

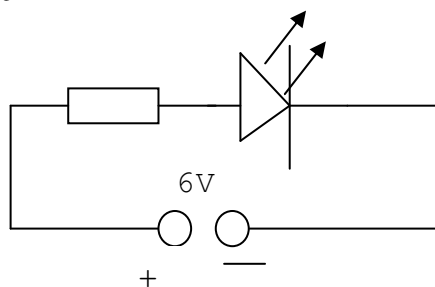

19. 400Ω

20. switch


21. base emitter collector

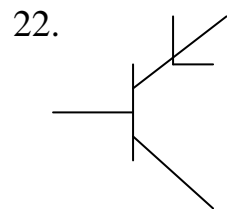

23. base and emitter


24. OR AND NOT

25.

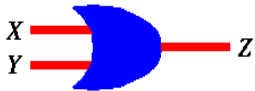


OR Gate Truth Table		
X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

AND

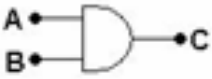

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

NOT



A	B
0	1
1	0

26. Truth tables show what the output will be for the various possible inputs

27.

input			output
A	B	C	
0	0	0	1
0	1	0	1
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	0
1	0	1	0
1	1	1	1

28. a clock

29. binary

30. eleven

31. LOW

32. Capacitor is uncharged to start

Voltage across capacitor is low

Voltage at output of NOT gate is HIGH

Capacitor charges through the resistor

Capacitor voltage increases and becomes High

Voltage at output to NOT gate becomes LOW

Capacitor discharges through resistor

Process repeats

Current is constantly changing direction – pulsing

33. increase resistance

increase capacitance

34. Amplifiers make signals bigger

35. The gain is how many times bigger the output signal is compared to the input signal

36. $\text{gain} = \frac{\text{output}}{\text{input}}$

37. there are no units for gain

38. a television and a radio

39. if the switch is closed the capacitor is charged
the voltage across the capacitor is high
the voltage across the base emitter terminals of the transistor is high
the transistor will conduct
the motor will be on

40.

