




Physics
Standard Grade


Unit 2
Using Electricity
General & Credit Past Paper
Questions

Record Sheet

| <u>General</u> - Section | Question | Attempted | RED | AMBER | GREEN |
|------------------------------|----------|-----------|-----|-------|-------|
| Multiple Choice | 1 | | | | |
| | 2 | | | | |
| 1. From the Wall Socket | 3 | | | | |
| | 4 | | | | |
| | 5 | | | | |
| 3. Resistance | 6 | | | | |
| | 7 | | | | |
| | 8 | | | | |
| | 9 | | | | |
| | 10 | | | | |
| 4. Useful Circuits | 11 | | | | |
| | 12 | | | | |
| | 13 | | | | |
| | 14 | | | | |
| | 15 | | | | |
| 5. Behind the Wall | 16 | | | | |
| | 17 | | | | |
| 6. Movement from Electricity | 18 | | | | |

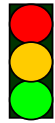

| <u>Credit</u> - Section | Question | Attempted | RED | AMBER | GREEN |
|------------------------------|----------|-----------|-----|-------|-------|
| 1. From the Wall Socket | 19 | | | | |
| | 20 | | | | |
| 2. AC & DC Currents | 21 | | | | |
| 3. Resistance | 22 | | | | |
| | 23 | | | | |
| | 24 | | | | |
| | 25 | | | | |
| | 26 | | | | |
| | 27 | | | | |
| | 28 | | | | |
| 4. Useful Circuits | 29 | | | | |
| | 30 | | | | |
| | 31 | | | | |
| 5. Behind the Wall | 32 | | | | |
| | 33 | | | | |
| | 34 | | | | |
| 6. Movement from Electricity | 35 | | | | |

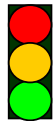

RED - I don't understand the question
I NEED HELP!

AMBER - I understand most of the question
I NEED TO REVISE A LITTLE MORE!

GREEN - I got the correct answer first time!!
I UNDERSTAND THIS TOPIC


General Level

Answer questions in your Homework Jotter.

Show working for each question.

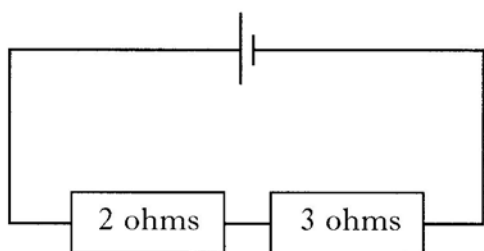1.

In the circuit shown, the current in the 2 ohm resistor is 1 ampere.




What is the current taken from the battery?

- A 0.4 ampere
- B 1 ampere
- C 2 amperes
- D 3 amperes
- E 5 amperes

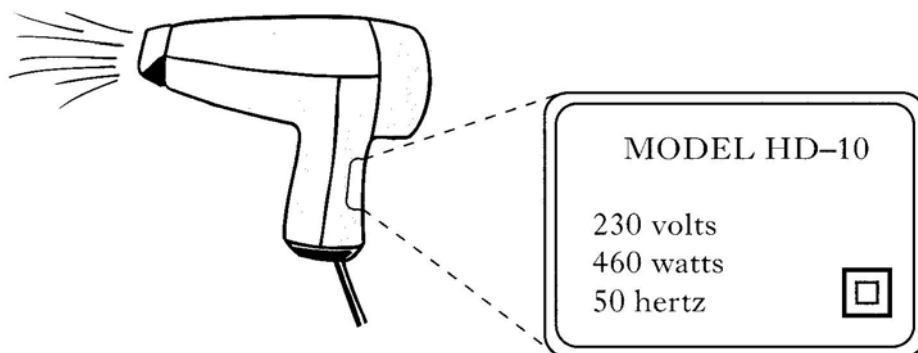3.


A hairdryer and its rating plate are shown below.



- (a) (i) How many wires are there in the flex of the hairdryer?
- (ii) State the name **and** the colour of insulation of each wire in the flex.
- (b) Calculate the current in the hairdryer when it is operating.
- (c) (i) State the correct fuse value for the plug of the hairdryer.
- (ii) What is the purpose of the fuse in the plug?

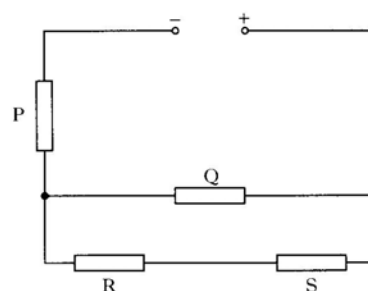2.

Four **identical** resistors, P, Q, R and S are connected as shown.



In which of the resistors is the current the same?

- A P and Q only
- B R and S only
- C P, R and S only
- D Q, R, and S only
- E P, Q, R and S

| KU | PS |
|----|----|
| 1 | |
| | 1 |
| | 1 |
| | 1 |
| | 1 |
| | 1 |
| | 1 |
| | 1 |


General Level

Answer questions in your Homework Jotter.

Show working for each question.

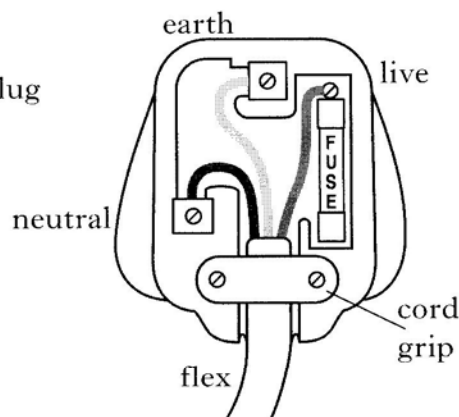4.

The flex of a mains appliance has a 3-pin plug fitted as shown.



The flex contains three wires—live, neutral and earth.

(a) Circle the correct answer for each of the questions about the wires.

(i) The colour of the insulation around the live wire is

- blue
- brown
- green/yellow

1

(ii) The colour of the insulation around the neutral wire is

- blue
- brown
- green/yellow

1


(iii) The $\left\{ \begin{array}{l} \text{earth} \\ \text{live} \\ \text{neutral} \end{array} \right\}$ wire is a safety device.

1

(b) **Explain** why the flex must be held in place by the cord grip.

2

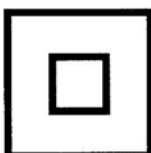(c) Another appliance has only two wires in its flex. This appliance carries the following symbol.



(i) Name this symbol.

1

(ii) Which wire is not needed in this flex?





1

| KU | PS |
|----|----|
| 1 | |
| 1 | |
| 1 | |
| 2 | |
| | 1 |
| 1 | |

General Level

Answer questions in your Homework Jotter.
Show working for each question.

5. Appliances convert electrical energy into other forms of energy.

| <i>Appliance</i> | <i>Rating plate</i> |
|---|--|
| Food processor  | <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 0 auto;"> 230 volts 50 hertz 400 watts </div> |
| Hair dryer  | <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 0 auto;"> 230 volts 50 hertz <div style="border: 2px solid black; width: 20px; height: 20px; margin: 0 auto;"></div> 1200 watts </div> |
| Kettle  | <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 0 auto;"> 230 volts 50 hertz 2200 watts </div> |
| Lamp  | <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 0 auto;"> 230 volts 50 hertz <div style="border: 2px solid black; width: 20px; height: 20px; margin: 0 auto;"></div> 60 watts </div> |

(a) State the **useful** energy output from the following appliances.

(i) Lamp: electrical energy \longrightarrow energy

(ii) Kettle: electrical energy \longrightarrow energy

(b) (i) Name **one** appliance from the table which requires an earth wire.

(ii) Circle **one** word or phrase in the passage below to make the statement correct.

The colouring of the insulation around the earth wire is

{

 blue
brown
green and yellow

}

(iii) Each appliance is fitted with either a 3 ampere or 13 ampere fuse. State the correct value of fuse for the following appliances.

(A) Lamp:.....

(B) Hair dryer:.....

| KU | PS |
|----|----|
| 1 | |
| 1 | |
| | 1 |
| 1 | |
| | 1 |
| | 1 |

General Level

Answer questions in your Homework Jotter.
Show working for each question.

7.

The following information is taken from a leaflet comparing conventional lamps with energy saving lamps.

A 20 watt energy saving lamp produces the same amount of light as a conventional 100 watt lamp.

Energy saving lamps can last 10 times as long as conventional lamps.

A conventional 100 watt lamp, used for an average of 4 hours per day, costs £1.00 per month to run.
An energy saving lamp producing the same amount of light, and used for the same time, costs 20 pence per month to run.

- (a) From the information given in the leaflet, state **one** advantage of using an energy saving lamp.
- (b) A householder replaces one conventional 100 watt lamp with a 20 watt energy saving lamp. It is used for an average of 4 hours per day. Calculate how much money is saved in running costs in one year.
- (c) The leaflet claims that the energy saving lamp is more energy efficient. Use information given to explain what this means.
- (d) The conventional lamp is a filament lamp.
The energy saving lamp is a discharge tube.
- (i) Where does the energy transformation take place in the conventional lamp?
- (ii) Where does the energy transformation take place in the energy saving lamp?


| KU | PS |
|----|----|
| | 1 |
| | 2 |
| | 2 |
| | 1 |
| | 1 |

General Level


Answer questions in your Homework Jotter.
Show working for each question.

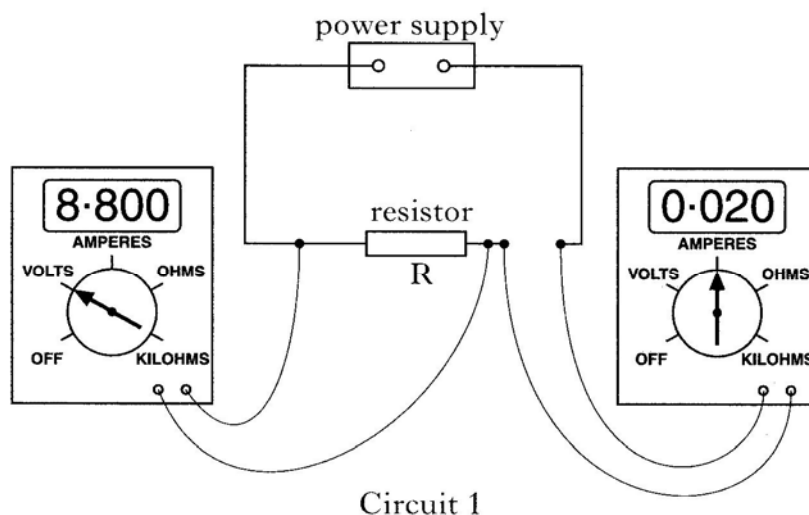8.

A student sets up circuit 1 to calculate the resistance of resistor R.



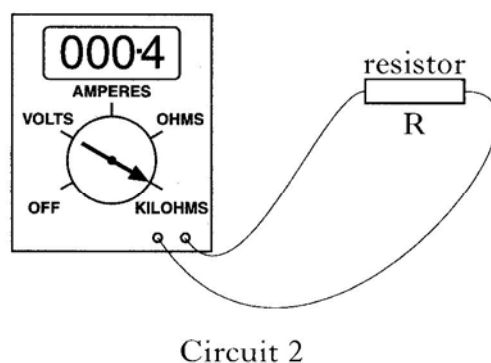- (a) Calculate the resistance of resistor R using the meter readings.
- (b) The student then sets up circuit 2 to measure the resistance of R directly.



Write down the resistance of R, **in ohms**, obtained from circuit 2.

- (c) The value obtained for the resistance of R using circuit 1 is more accurate than the value obtained using circuit 2.
- (i) Explain why circuit 1 gives a more accurate value for the resistance of R.
- (ii) What change could be made in circuit 2 to give a more accurate value for the resistance of R?

| KU | PS |
|----|----|
| | 2 |
| | 1 |
| | 1 |


General Level

Answer questions in your Homework Jotter.

Show working for each question.


9. A model car contains an electric motor, operated by a 6 volt battery. The speed of the motor is adjusted by a hand-held control. The hand-held control contains a variable resistor.

The circuit is shown below.

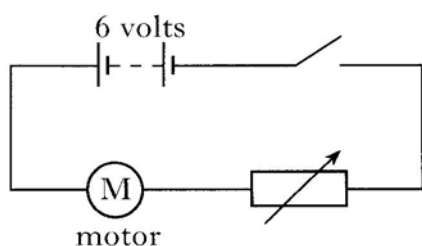

- (a) When the resistance of the variable resistor is set to 8 ohms, the voltage across the variable resistor is 2 volts.
- (i) Calculate the current in the variable resistor.
 - (ii) Calculate the voltage across the motor at this setting of the variable resistor.
- (b) The resistance of the variable resistor is decreased.
Explain what happens to the speed of the motor.
- (c) Give one **other** use for a variable resistor.

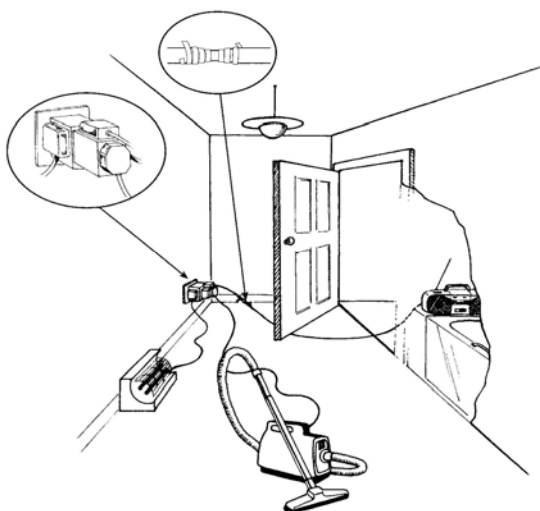10. There are several electrical hazards shown in the picture.



Identify **two** of the electrical hazards shown and for each explain why it is dangerous.

Hazard 1

Give reason why it is dangerous.

Hazard 2

Give reason why it is dangerous



| KU | PS |
|----|----|
| 2 | 1 |
| 2 | 2 |
| 1 | 1 |
| 4 | 4 |

General Level

Answer questions in your Homework Jotter.

Show working for each question.

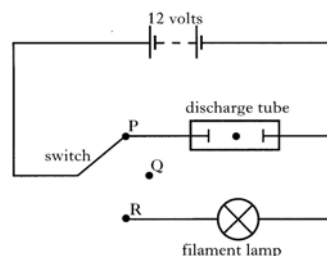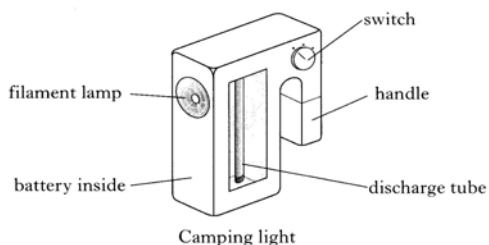11. A camping light contains an 8 watt discharge tube, an 8 watt filament lamp and a 12 volt battery.




The circuit diagram for the camping light is shown.

Write down the correct letter for each of the questions about the camping light

- (a) The camping light is **off** when the switch is in position $\left\{ \begin{array}{c} P \\ Q \\ R \end{array} \right\}$

- (b) The operating voltage of the filament lamp is $\left\{ \begin{array}{c} 6 \\ 8 \\ 12 \end{array} \right\}$ volts.

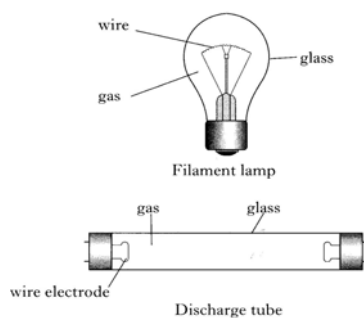- (c) The filament lamp and the discharge tube are constructed as shown below.



- (i) The useful energy transformation in the filament lamp takes place in the { **glass wire gas** }
- (ii) The useful energy transformation in the discharge tube takes place in the { **glass wire gas** }
- (iii) The electrical energy transformed each second by the discharge tube is { **smaller than the same as greater than** } the electrical energy transformed each second by the filament lamp.
- (iv) The heat energy produced each second by the discharge tube is { **smaller than the same as greater than** } the heat energy produced each second by the filament lamp.

| KU | PS |
|----|----|
| 1 | 1 |
| 1 | 1 |
| 1 | 1 |
| 1 | 1 |


General Level

Answer questions in your Homework Jotter.

Show working for each question.

12.

(a) Three identical lamps are shown in Circuit 1 below.

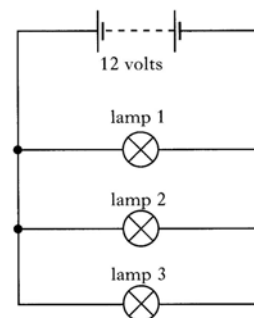


Circuit 1

- (i) The battery has a voltage of 12 volts and supplies a current of 0.9 ampere to the circuit.

Complete the table below to show the current in each lamp and the voltage across each lamp.

| | <i>Lamp 1</i> | <i>Lamp 2</i> | <i>Lamp 3</i> |
|--------------------------|---------------|---------------|---------------|
| <i>Current</i> (amperes) | | | |
| <i>Voltage</i> (volts) | | | |

- (ii) The three lamps and battery are now reconnected as shown in Circuit 2 below. The current from the battery is now 0.1 ampere.

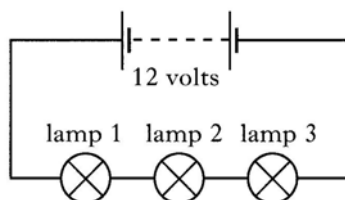

Circuit 2

Complete the table below to show the current in each lamp and the voltage across each lamp.

| | <i>Lamp 1</i> | <i>Lamp 2</i> | <i>Lamp 3</i> |
|--------------------------|---------------|---------------|---------------|
| <i>Current</i> (amperes) | | | |
| <i>Voltage</i> (volts) | | | |

- (b) (i) Which of the circuits, Circuit 1 or Circuit 2, shown in (a) is similar to a household lighting circuit?
- (ii) Name an electrical appliance used in the home that requires two or more switches to be used in series.

| KU | PS |
|----|----|
| 1 | 1 |
| 1 | 1 |
| 1 | 1 |
| 1 | 1 |


General Level

Answer questions in your Homework Jotter.

Show working for each question.

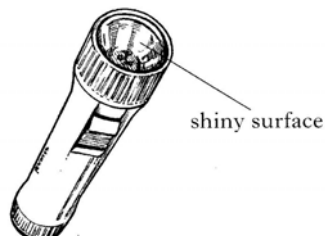13.

A torch contains a battery, a lamp and a switch connected in series.



- (a) Draw the circuit diagram for the torch, using the correct symbols.
- (b) Complete the passage below, using words from the following list.

voltage current charge


When the torch is on, moves around the circuit.

This movement is called a

- (c) What is the **useful** energy transformation that takes place in the lamp when the torch is on?
- (d) Why is the surface behind the lamp shiny?

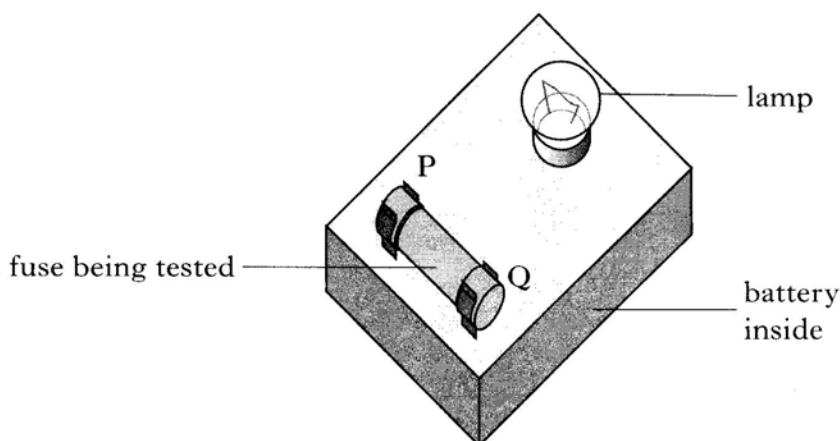14.

A continuity tester is used to test if a fuse has “blown”. The continuity tester contains a lamp and a 1.5 volt battery.



- a) Draw the circuit diagram for the continuity tester.
On your diagram, include the fuse being tested between points P and Q .
You must use correct circuit symbols for all components.
- b) Describe how the continuity tester is used to show that the fuse being tested is 'blown'.

| KU | PS |
|----|----|
| | 3 |
| | 2 |
| | 1 |
| | 1 |
| | 4 |
| | 3 |

General Level


Answer questions in your Homework Jotter.
Show working for each question.

16. (continued)

- (ii) (A) All the lamps are switched on for a tennis match. The match lasts for 3 hours.
Calculate how many kilowatt-hours of electrical energy are used during this match.
- (B) The cost of 1 kilowatt-hour of electrical energy is 5 pence.
Calculate the cost of the energy used for the lighting during this match.
- (d) A fuse is included in the floodlight circuit to protect the wiring.
Name **one** other device that could be used instead of a fuse.

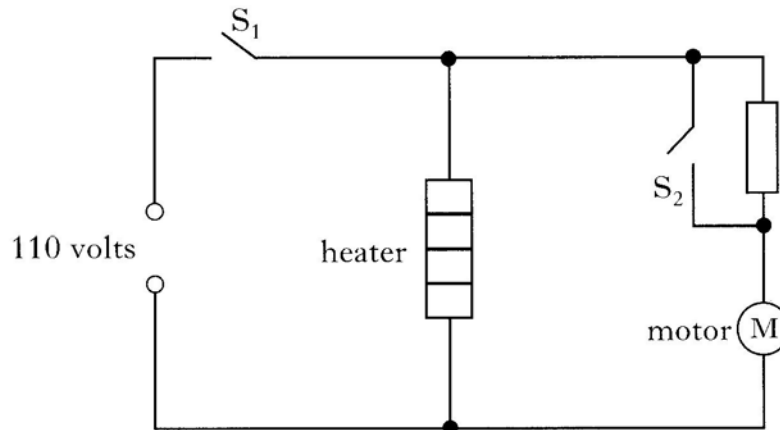17.

A two-speed hot air blower is used in a factory. The blower operates from a 110 volt supply. The blower contains a heater, and a fan attached to a motor. The blower is switched on by closing switch S_1 .



- (a) What is the voltage across the heater when the blower is operating?
- (b) Explain why switch S_2 should now be closed for the blower to operate at high speed.
- (c) When operated at high speed, the blower is rated at 2000 watts. The blower is operated at high speed for 8 hours.
- (i) Calculate the number of kilowatt-hours of energy it uses in this time.
- (ii) Electricity costs 9 pence per kilowatt-hour.
Calculate the cost of operating the blower for 8 hours.

| KU | PS |
|----|----|
| | 1 |
| | 2 |
| 1 | |
| | 1 |
| | 2 |
| | 2 |
| | 2 |


Credit Level

Answer questions in your Homework Jotter.

Show working for each question.

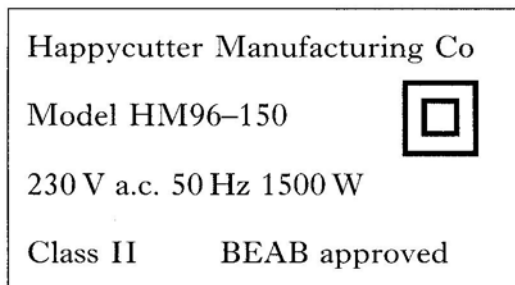
19.

A lawnmower has a label which gives the following information.



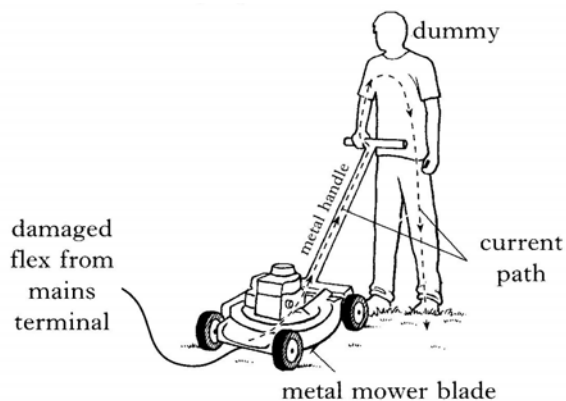- (a) (i) State why this lawnmower has only two wires in the flex.
- (ii) State the colours of the insulation on the two wires in the flex.
- (iii) State the value of the fuse that should be fitted in the plug of this lawnmower.
- (b) Care must be taken to make sure that the lawnmower does not cut its own flex. When this happens, there is a current path from the damaged flex, through the metal handle and the person using the lawnmower, to earth.

A dummy is used to investigate the safety of this lawnmower. In one test, the resistance of the current path through the dummy is $5000\ \Omega$. This is approximately the same resistance as the current path when the lawnmower is used by a person.



- (i) Show by calculation that the current which passes through the dummy is 46 mA.
- (ii) Explain why, in a situation like this, the fuse in the plug **would not** protect a person using the lawnmower.
- (iii) What is the purpose of the fuse in the plug?
- (iv) Water is now sprayed on the dummy and the investigation repeated. State and explain the effect that this has on the current through the dummy.

| KU | PS |
|----|----|
| 1 | |
| | 2 |
| 1 | |
| | |
| | |
| | |
| 2 | |
| | 2 |
| | |
| 1 | |
| | |
| | |
| | 2 |


Credit Level

Answer questions in your Homework Jotter.
Show working for each question.

| KU | PS |
|----|----|
| | 1 |
| | 3 |
| | 1 |
| | 1 |
| | 1 |

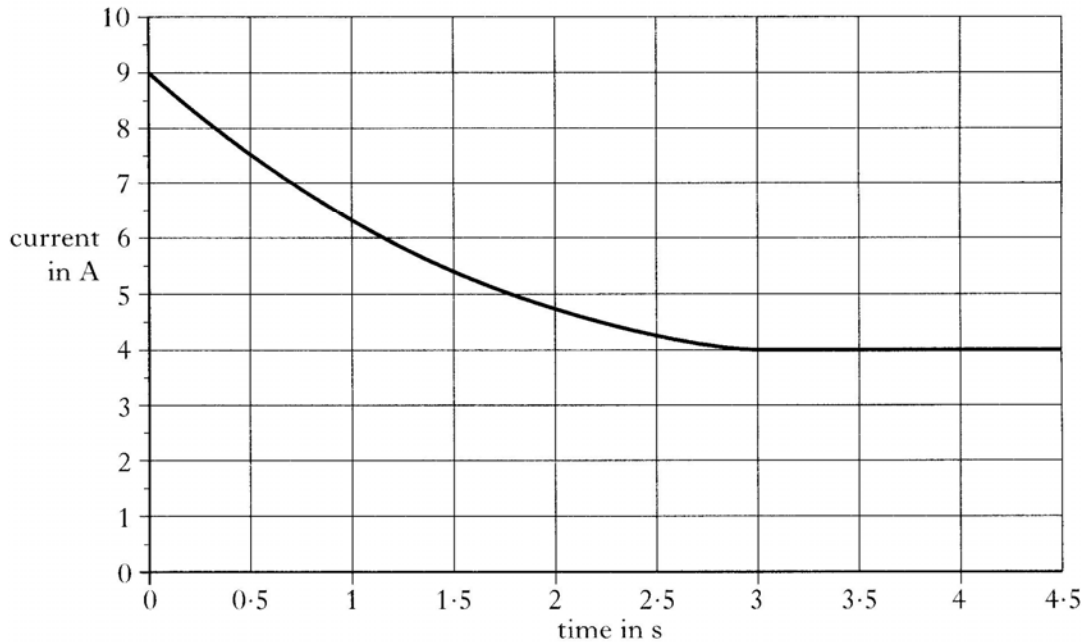20.

A mains vacuum cleaner contains a motor that takes 3.0 s to reach full speed after being switched on. The graph shows how the current in the motor varies from the time the motor is switched on.



- (a) (i) State the current when the motor has reached full speed. 1
- (ii) Calculate the power of the motor when it has reached full speed. 3
- (b) The vacuum cleaner is connected to the mains supply by a flex fitted with a fused plug.
- (i) All the fuses shown are available. 1

3 ampere

5 ampere

10 ampere

13 ampere

Which one of these fuses is **most** suitable for fitting in the plug?

- (ii) State the purpose of the fuse fitted in the plug. 1
- (iii) Explain why the fuse must be connected in the live wire. 1


Credit Level

Answer questions in your Homework Jotter.

Show working for each question.

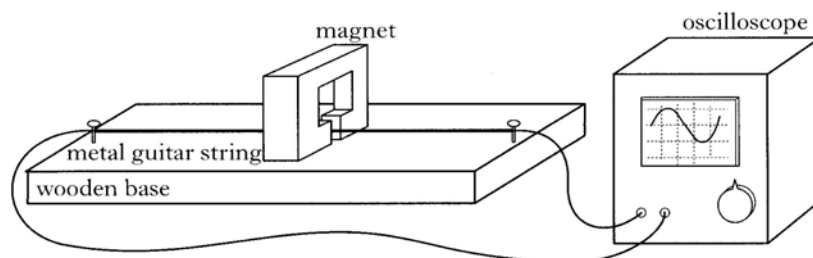21.

A metal guitar string, fixed to a wooden base, is connected to an oscilloscope. A magnet is placed so that the string is between the poles of the magnet, as shown.




When the string is plucked, a sound is produced and a voltage is induced in the string. The induced voltage is displayed on the screen of the oscilloscope.

- (a) (i) Why is a voltage induced when the string is plucked?
 (ii) State one change that can be made so that a larger voltage is induced.

- (b) The oscilloscope gain setting and trace are shown.


Calculate the peak voltage.

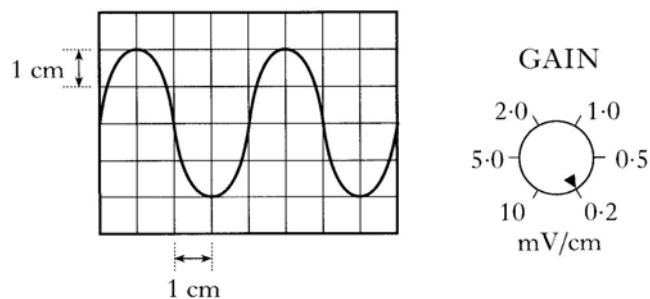


- (c) A different metal string is used to produce a louder sound of higher frequency. No other changes are made to the equipment.

Draw a possible new trace on a grid in your jotter.

trace produced
by original
string

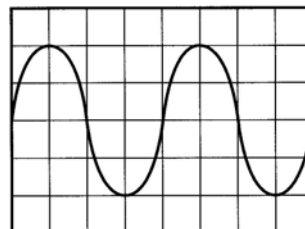

trace produced
by second
string

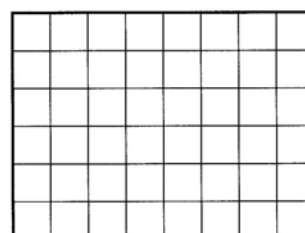


| KU | PS |
|----|----|
| 1 | |
| 1 | |
| | 2 |
| | 2 |

Credit Level

Answer questions in your Homework Jotter.
Show working for each question.

25. (Continued)

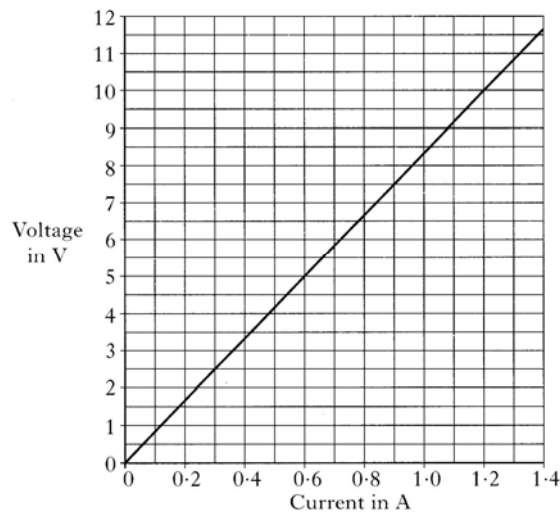


- (i) Calculate the resistance of component X when the current is 1.2 A.

(You must use an appropriate number of significant figures in your answer to this question.)

- (ii) Using information from the graph, explain what happens to the resistance of component X as the current is increased.

Justify your answer by calculation or otherwise.

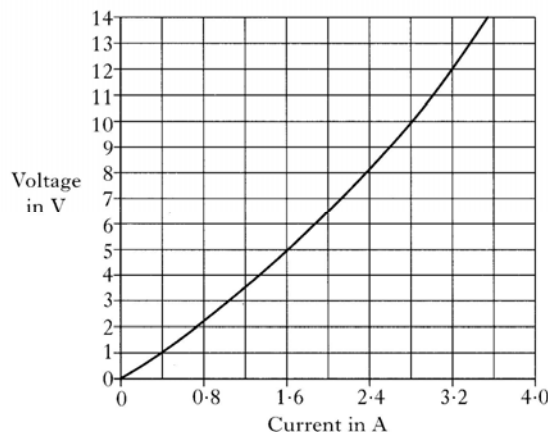- (b) The student replaces component X with component Y, repeats the experiment and obtains the following graph.



- (i) The student concludes that the resistance of component Y is not constant. Why is the student correct in coming to this conclusion?
- (ii) (A) From the graph, what is the current in component Y when the voltage across component Y is 12 V?
- (B) Calculate the power dissipated in component Y when the voltage across it is 12 V.

| KU | PS |
|----|----|
| | |
| | 2 |
| | 3 |
| | 1 |
| | 1 |
| 2 | |

Credit Level


Answer questions in your Homework Jotter.

Show working for each question.

27.

Two students are investigating voltage, current and resistance.

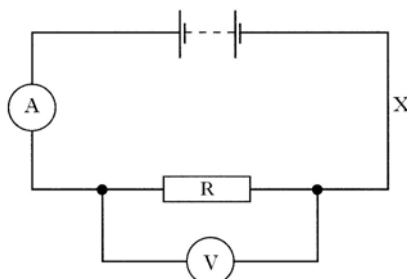(a) The first student builds the circuit shown.




The ammeter displays a current of 0.10 A and the voltmeter displays a voltage of 3.0 V.

- (i) Calculate the resistance of R when the current is 0.10 A.
- (ii) The student inserts another ammeter at position X.

What is the reading on this ammeter?

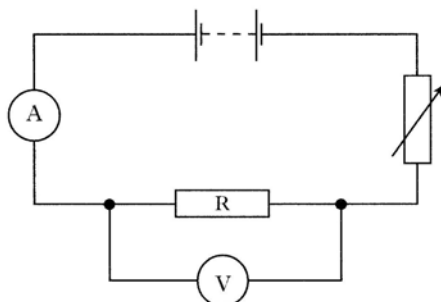(b) The second student uses the **same** resistor in the circuit below.



This student obtains the following set of results.

| Result number | Voltage across R (V) | Current through R (A) |
|---------------|----------------------|-----------------------|
| 1 | 6.0 | 0.20 |
| 2 | 7.5 | 0.25 |
| 3 | 9.0 | 0.30 |
| 4 | 10.0 | 0.35 |
| 5 | 12.0 | 0.40 |

- (i) Describe how these different values of voltage and current are obtained.
 - (ii) Explain which result should be retaken.
- (c) What additional information about resistance does the second student's experiment give compared to the first student's experiment?

| KU | PS |
|----|----|
| | |
| 2 | |
| | 1 |
| | |
| | 2 |
| | 2 |
| | 1 |

Credit Level

Answer questions in your Homework Jotter.

Show working for each question.

28.

Two groups of pupils are investigating the electrical properties of a lamp.

(a) Group 1 is given the following equipment:

ammeter; voltmeter; 12 V d.c. supply; lamp; connecting leads.

Complete the circuit diagram to show how this equipment is used to measure the current through, and the voltage across, the lamp.



(b) Group 2 uses the same lamp and is only given the following equipment:

lamp; ohmmeter; connecting leads.

What property of the lamp is measured by the ohmmeter?

(c) The results of both groups are combined and recorded in the table below.

| I(A) | V(V) | R(Ω) | IV | I^2R |
|------|------|---------------|----|--------|
| 2 | 12 | 6 | | |

- (i) Use these results to complete the last two columns of the table.
- (ii) What quantity is represented by the last two columns of the table?
- (iii) What is the unit for this quantity?

| KU | PS |
|----|----|
| 3 | 1 |
| 1 | 2 |
| 1 | 1 |


Credit Level

Answer questions in your Homework Jotter.


Show working for each question.

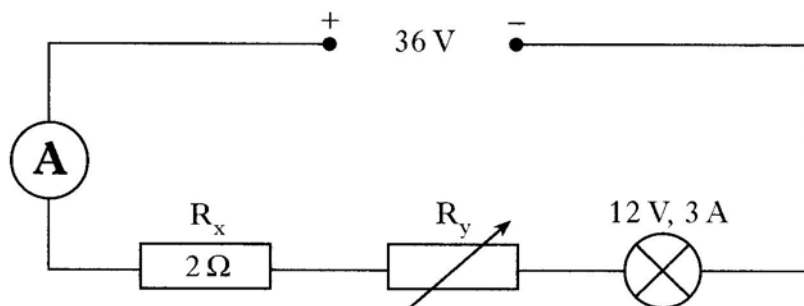29.

A student designs the circuit shown to operate a 12 V, 3 A lamp from a 36 V supply.



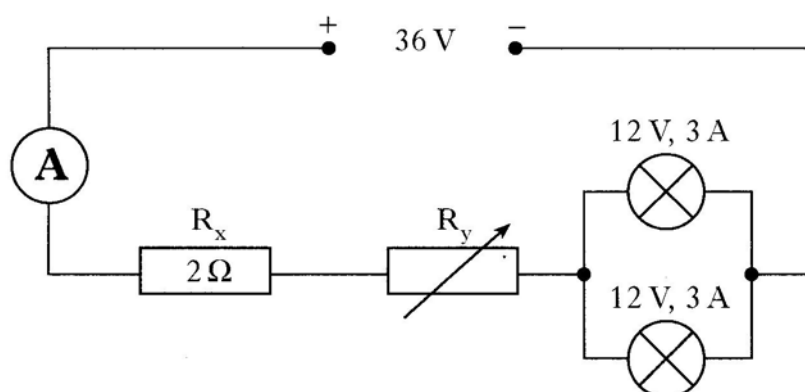- (a) What is the reading on the ammeter when the lamp is operating at its correct power rating?
- (b) The resistance of R_x is $2\ \Omega$.
Calculate the voltage across R_x when the lamp is operating correctly.
- (c) Calculate the resistance of R_y when the lamp is operating correctly.
- (d) The student connects a second, identical lamp as shown in the diagram below.



Explain why the resistance of R_y has to be adjusted for both lamps to operate correctly.


| KU | PS |
|----|----|
| | 1 |
| | 2 |
| | 3 |
| | 2 |

Credit Level

Answer questions in your Homework Jotter.
Show working for each question.

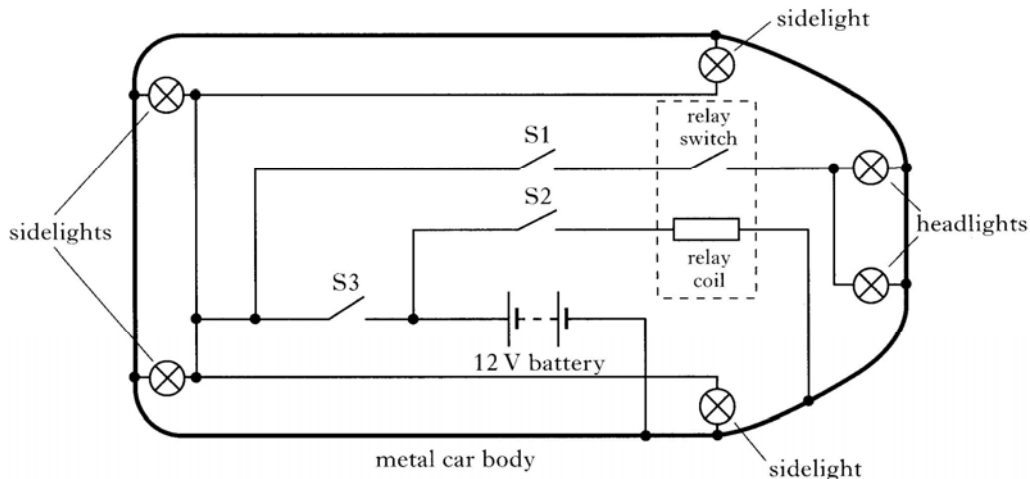30.

The circuit diagram of the wiring of a car's sidelights and headlights is shown.



S1 is the headlight switch. S2 is the ignition switch.

When there is a current in the relay coil, the relay switch closes.

(a) Which lights are on when switch S3 **only** is closed?

(b) At night the car has the sidelights on and the headlights on. The driver switches off the ignition. This opens the ignition switch.

Explain why **only** the headlights go out.

(c) **Each** sidelight is rated at 12 V, 6 W, and **each** headlight is rated at 12 V, 55 W.

- (i) Calculate the current in the battery when **only** the sidelights are on.
- (ii) The driver leaves the car for 10 minutes with **only** the sidelights on. Calculate the charge that flows through the battery in this time.
- (iii) Each headlight gives out more light energy than each sidelight when on for the same time. Explain why this happens.

| KU | PS |
|----|----|
| | 1 |
| | 2 |
| | 3 |
| | 2 |
| | 2 |

Credit Level


Answer questions in your Homework Jotter.
Show working for each question.

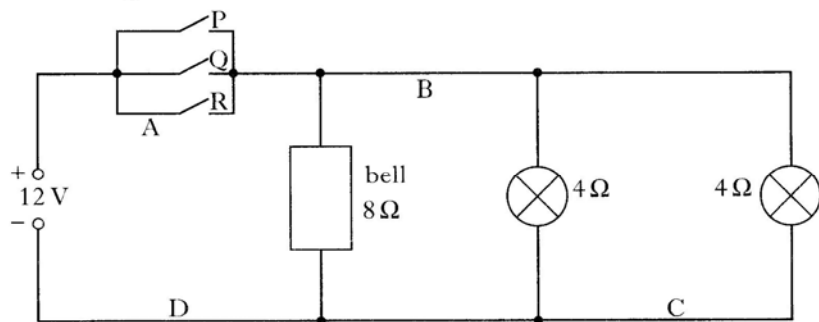31.

A post office contains an emergency alarm circuit. Each of three cashiers has an alarm switch fitted as shown. Lamps come on and a bell sounds if an alarm switch is closed.



The circuit diagram for the alarm is shown.



- (a) The alarm circuit is to be controlled by a master switch.
Which position, A, B, C or D, is most suitable for the master switch?
- (b) Each lamp has a resistance of 4Ω and the bell has a resistance of 8Ω .
The circuit uses a 12 V supply.
- (i) Calculate the total resistance of the alarm circuit.
- (ii) Calculate the current from the supply when the alarm is operating.
- (c) Brighter lamps are fitted in the alarm circuit.
Explain how this change affects the resistance of the circuit.

| KU | PS |
|----|----|
| | 1 |
| | 2 |
| | 2 |
| | 2 |


Credit Level

Answer questions in your Homework Jotter.

Show working for each question.

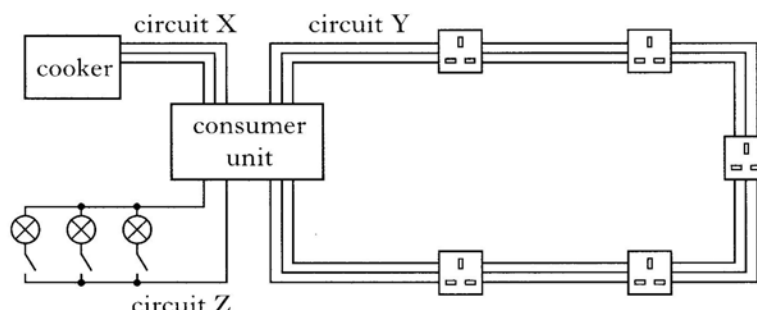32.


The diagram shows three household circuits, connected to a consumer unit.



- (a) (i) Which circuit is a ring circuit? 1
- (ii) Give **two** advantages of using a ring circuit. 2
- (b) State and explain **one** difference between a lighting circuit and a ring circuit. 2
- (c) (i) Why does a cooker need a separate circuit? 1
- (ii) One heating element of the cooker has a power rating of 2.2 kW. Calculate how many joules of energy are transferred by this element in 2 hours. 2
- (d) (i) What is the purpose of an earth wire? 1
- (ii) Explain how an earth wire works. 2

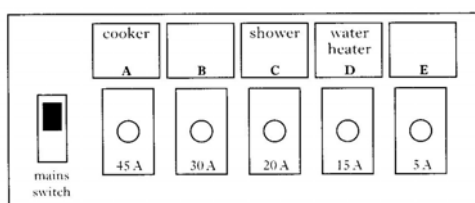33.

The consumer unit in a house contains a mains switch and circuit breakers for different circuits.



- (a) (i) What is the purpose of the mains switch? 1
- (ii) Two of the circuits have not been labelled. Which circuit is: the ring circuit? the lighting circuit? 1
- (iii) The current ratings for the ring circuit and the lighting circuit are different. State another difference between the ring circuit and the lighting circuit. 1
- (b) (i) A 25 W lamp is designed to be used with mains voltage. Calculate the resistance of the lamp. 3
- (ii) Four of these lamps are connected in parallel. Calculate the **total** resistance of the lamps. 2


| KU | PS |
|----|----|
| 1 | |
| 2 | |
| | 2 |
| | 1 |
| | 2 |
| 1 | |
| 2 | |
| | 1 |
| | 1 |
| | 1 |
| | 3 |
| 2 | |

Credit Level


Answer questions in your Homework Jotter.
Show working for each question.

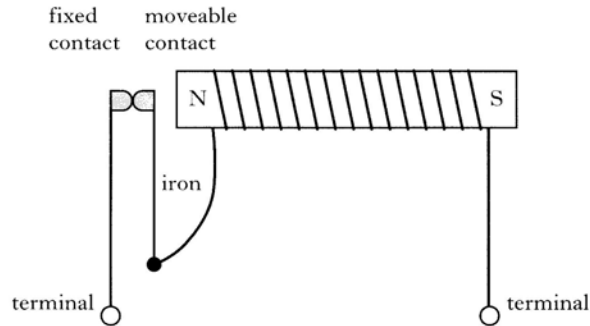34.

A circuit breaker as shown below is used in a circuit.




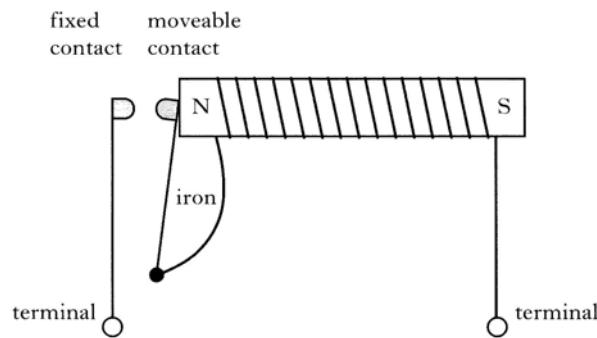- (a) (i) State **one** advantage of a circuit breaker compared to a fuse.
 (ii) The circuit breaker breaks the circuit when the current becomes too high.



Explain how the circuit breaker operates when the current becomes too high.

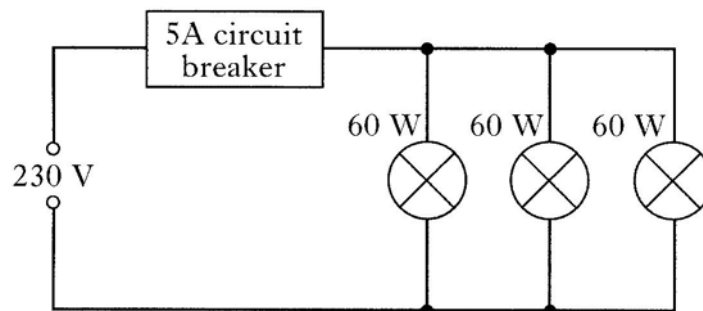- (b) A 5 ampere circuit breaker is used in a household lighting circuit which has three 60 W lamps as shown below.



- (i) Show that the resistance of **one** lamp is 882Ω .
 (ii) Calculate the combined resistance of the three lamps in this circuit.
 (iii) Show by calculation whether the circuit breaker will switch off the lamps when all three are lit.

| KU | PS |
|----|----|
| 1 | |
| | 2 |
| | 2 |
| | 3 |

Credit Level

Answer questions in your Homework Jotter.

Show working for each question.

35.

A simple d.c. motor is shown in Figure 1.

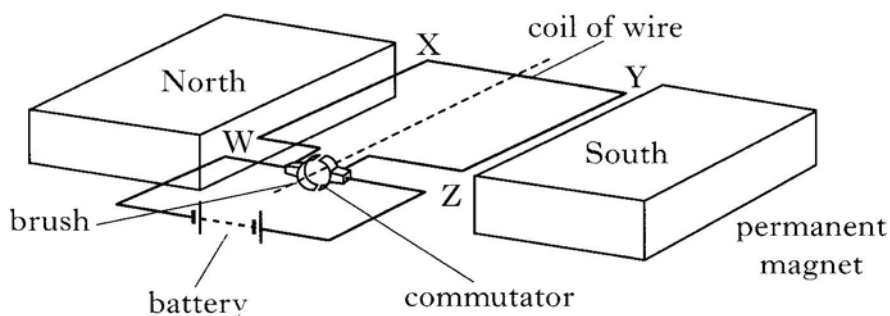


Figure 1

(a) The coil WXYZ rotates in a clockwise direction.

State **two** changes that could be made to make the coil rotate in the opposite direction.

(b) Part of a commercial electric motor is shown in Figure 2.

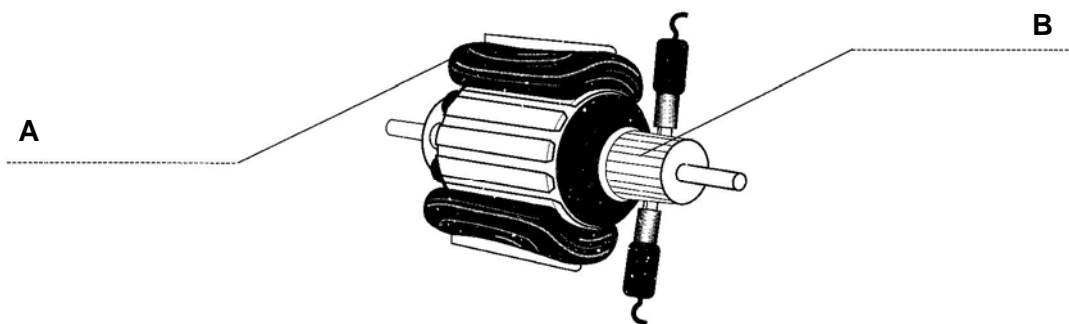


Figure 2

(i) Label the two parts indicated on the motor, using names from the list below.

- brush commutator field coil rotating coil**

(ii) In the commercial electric motor, state why

(A) more than one rotating coil is used

(B) field coils rather than permanent magnets are used.

| KU | PS |
|----|----|
| | |
| 2 | |
| 2 | |
| 1 | |
| 1 | |

SQA Source Papers

| <u>General</u> - Section | | Paper | Question |
|------------------------------|----|-------|----------|
| Multiple Choice | 1 | 2000 | 1 |
| | 2 | 2007 | 2 |
| 1.From the Wall Socket | 3 | 2002 | 11 |
| | 4 | 2006 | 9 |
| | 5 | 2007 | 7 |
| 3. Resistance | 6 | 2000 | 9 |
| | 7 | 2003 | 9 |
| | 8 | 2003 | 10 |
| | 9 | 2004 | 8 |
| | 10 | 2004 | 10 |
| 4. Useful Circuits | 11 | 2000 | 8 |
| | 12 | 2001 | 9 |
| | 13 | 2002 | 10 |
| | 14 | 2003 | 11 |
| | 15 | 2007 | 9 |
| 5. Behind the Wall | 16 | 2001 | 10 |
| | 17 | 2005 | 9 |
| 6. Movement from Electricity | 18 | 2004 | 9 |

| <u>Credit</u> - Section | | Paper | Question |
|------------------------------|----|-------|----------|
| 1.From the Wall Socket | 19 | 2000 | 4 |
| | 20 | 2005 | 4 |
| 2. AC & DC Currents | 21 | 2004 | 10 |
| 3. Resistance | 22 | 2000 | 3 |
| | 23 | 2001 | 2 |
| | 24 | 2001 | 3 |
| | 25 | 2002 | 3 |
| | 26 | 2003 | 3 |
| | 27 | 2006 | 3 |
| | 28 | 2007 | 5 |
| 4. Useful Circuits | 29 | 2003 | 6 |
| | 30 | 2004 | 4 |
| | 31 | 2005 | 5 |
| 5. Behind the Wall | 32 | 2002 | 4 |
| | 33 | 2007 | 4 |
| | 34 | 2006 | 4 |
| 6. Movement from Electricity | 35 | 2001 | 4 |