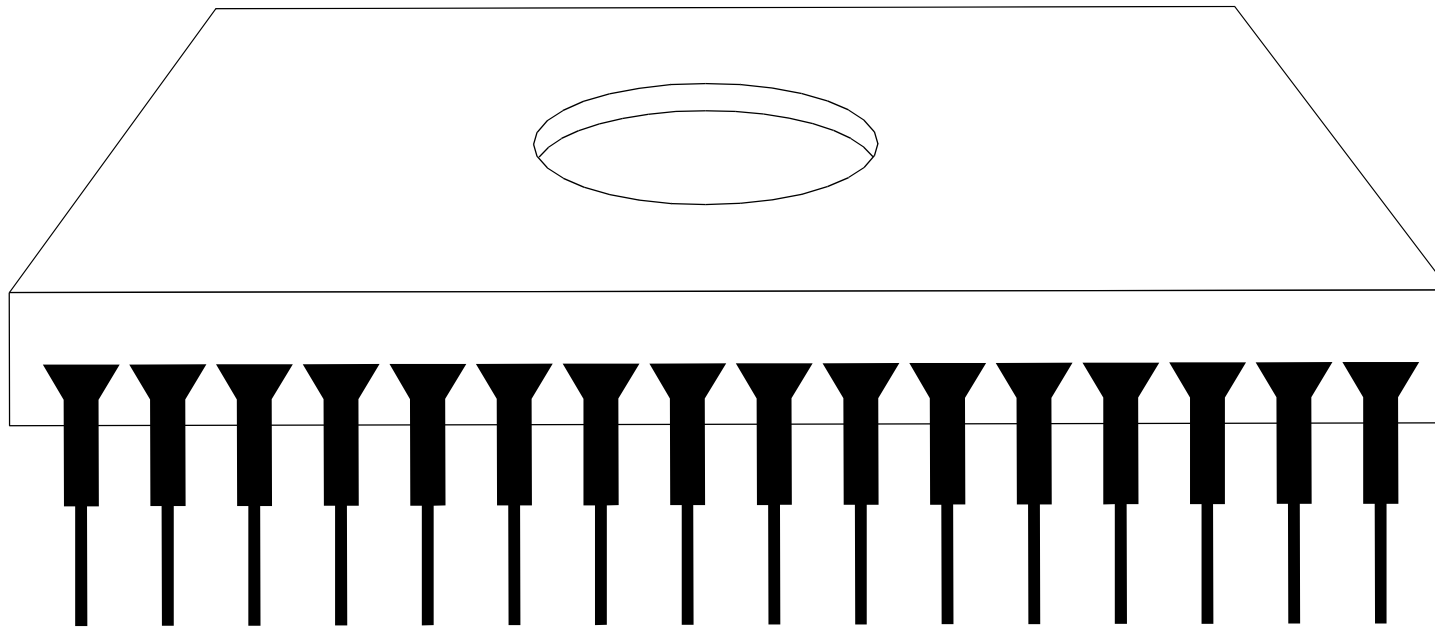


# Standard Grade Physics

## "ELECTRONICS"



Name: \_\_\_\_\_ Class: \_\_\_\_\_ Teacher: \_\_\_\_\_

# LEARNING OUTCOMES

blue = General

red = Credit

1) Electronic Systems Overview							
1.	I can state that an electronic system consists of three parts - input, process and output.						
2.	I can distinguish between analogue and digital signals.						
3.	I can identify analogue and digital signals from waveforms viewed on an oscilloscope.						

2) Input Devices							
1.	I can describe the energy transformations involved in a microphone, thermocouple and solar cell.						
2.	I can state that the resistance of a thermistor changes with temperature and the resistance of an LDR decreases with increasing light intensity (and vice versa).						
3.	I can carry out calculations using voltage, current and resistance for a thermistor and LDR.						
4.	I can carry out calculations involving voltages and resistances in a voltage divider.						
5.	I can state that during charging, the voltage across a capacitor increases with time.						
6.	I can state that the time to charge a capacitor depends on the values of the capacitance and series resistance.						
7.	I can identify, from a list, an appropriate input device for a given application.						
8.	I can identify, without a list, appropriate input devices for a given application.						

3) Output Devices							
1.	I can give examples of output devices and the energy conversions involved.						
2.	I can give examples of analogue output devices and digital output devices.						
3.	I can draw and identify the symbol for an LED.						
4.	I can state that an LED will light only if connected one way round.						
5.	I can explain the need for a series resistor with an LED.						
6.	I can describe, by means of a diagram, a circuit which will allow an LED to light.						
7.	I can state that different numbers can be produced by lighting appropriate segments (LED's) of a 7-segment display.						
8.	I can calculate the value of the series resistor for an LED.						
9.	I can identify appropriate output devices for a given application.						

	4) Digital Process Devices						
1.	I can state that logic gates may have one or more inputs and that a truth table shows the output for all possible input combinations.						
2.	I can draw and identify the symbols for two input AND and OR gates, and a NOT gate (inverter).						
3.	I can state that: <ul style="list-style-type: none"> <li>● high voltage = logic '1'</li> <li>● low voltage = logic '0'.</li> </ul>						
4.	I can draw the truth tables for two input AND and OR gates, and a NOT gate (inverter).						
5.	I can identify the following logic gates from truth tables: <ul style="list-style-type: none"> <li>● two-input AND</li> <li>● two-input OR</li> <li>● NOT (inverter)</li> </ul>						
6.	I can complete a truth table for a simple combinational logic circuit.						
7.	I can explain how to use combinations of digital logic gates for control in simple situations.						
8.	I can state that a digital circuit can produce a series of clock pulses.						
9.	I can explain how a simple oscillator (clock pulse generator) built from a resistor, capacitor and inverter works.						
10.	I can describe how to change the frequency of the clock pulses produced by a simple oscillator (clock pulse generator).						
11.	I can state that there are circuits which can count digital pulses.						
12.	I can give an example of a device containing a counter circuit.						
13.	I can state that the output of the counter circuit is in binary.						
14.	I can state that the output of a binary counter circuit can be converted to decimal.						
15.	I can calculate the decimal equivalent of a binary number in the range 0000 - 1001.						
16.	I can draw and identify the circuit symbol for an NPN transistor.						
17.	I can state that a transistor may be conducting (ON) or non-conducting (OFF).						
18.	I can state that a transistor can be used as a switch.						
19.	I can identify, from a circuit diagram, the purpose of a simple transistor switching circuit.						
20.	I can explain the operation of a simple transistor switching circuit.						

	<b>5) Analogue Process Devices - Amplifiers</b>						
<b>1.</b>	I can identify, from a list, devices in which amplifiers play an important part.						
<b>2.</b>	I can state the function of the amplifier in devices such as radios, intercoms and music centres.						
<b>3.</b>	I can state that the output signal of an audio amplifier has the same frequency as the input signal, but has a larger amplitude.						
<b>4.</b>	I can carry out calculations involving input voltage, output voltage and voltage gain of an amplifier.						
<b>5.</b>	I can describe how to measure the voltage gain of an amplifier.						
<b>6.</b>	I can carry out calculations involving power, voltage and resistance (impedance).						
<b>7.</b>	I can carry out calculations involving input power, output power and power gain of an amplifier.						

# 1) ELECTRONIC SYSTEMS OVERVIEW

Any **electronic system** consists of **3 parts**:



**Information** is passed along the system by \_\_\_\_\_.

The table shows examples of **electronic systems** and their **input**, **process** and **output** parts:

system	input	process	output
CD player			
electronic calculator			
electronic stopwatch			
computer			
radio			

## The Electrical Signals

The **electrical signals** are either **analogue** or **digital**.

### Analogue Signals

These can have many \_\_\_\_\_ values.

Often, their value keeps \_\_\_\_\_.







### Digital Signals

These have only **2** values.

We describe these values in different ways:

\_\_\_\_\_/\_\_\_\_\_ or \_\_\_\_/\_\_\_\_ or \_\_\_\_/\_\_\_\_

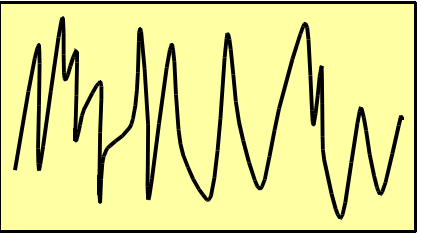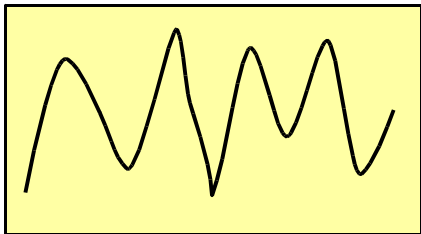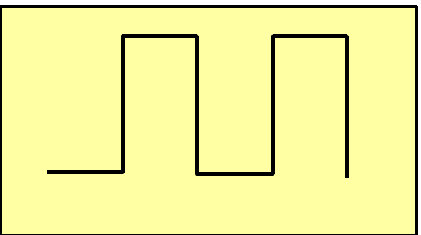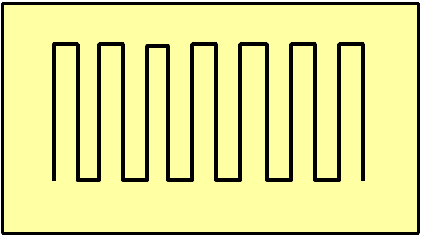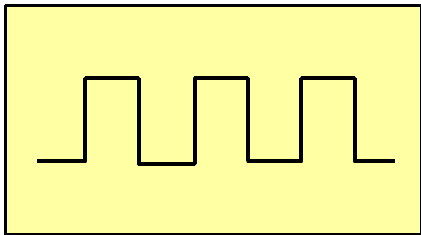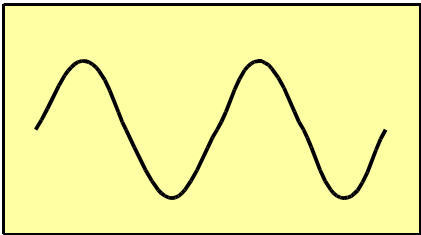
Are these signals on an oscilloscope **analogue** or **digital**?



## 2) INPUT DEVICES

**Input devices** measure the **energy** surrounding them and change it into **electrical energy**.

For example:

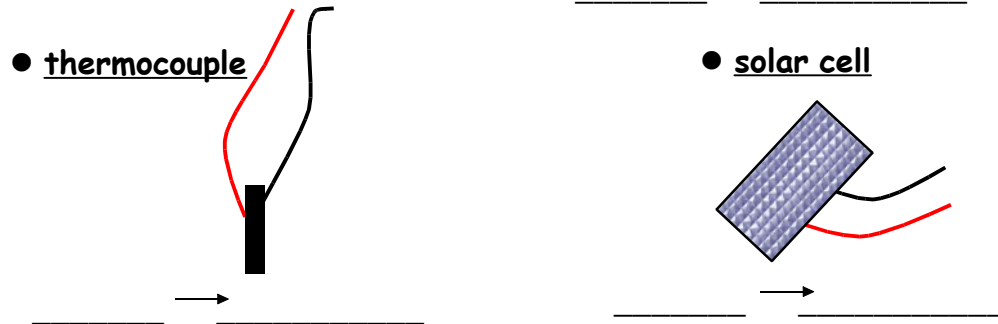

The **electrical energy** is in the form of a **changing voltage**.

The **resistance** of some **input devices** changes as the **energy** they measure changes.


For example:

• **thermistor**




The **resistance** of a **thermistor** changes as its \_\_\_\_\_ changes.

• **light dependent resistor (LDR)**

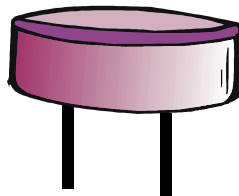


The **resistance** of a **LDR** \_\_\_\_\_ as the **light level** \_\_\_\_\_ (and vice versa).

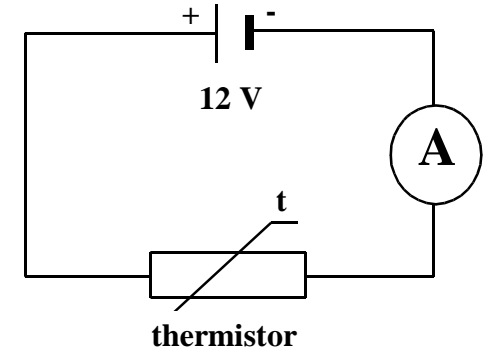The **thermistor** in this circuit controls the size of the **current** flowing around the circuit. As the **temperature** changes, the **resistance** of the **thermistor** changes, so the size of the **current** changes.



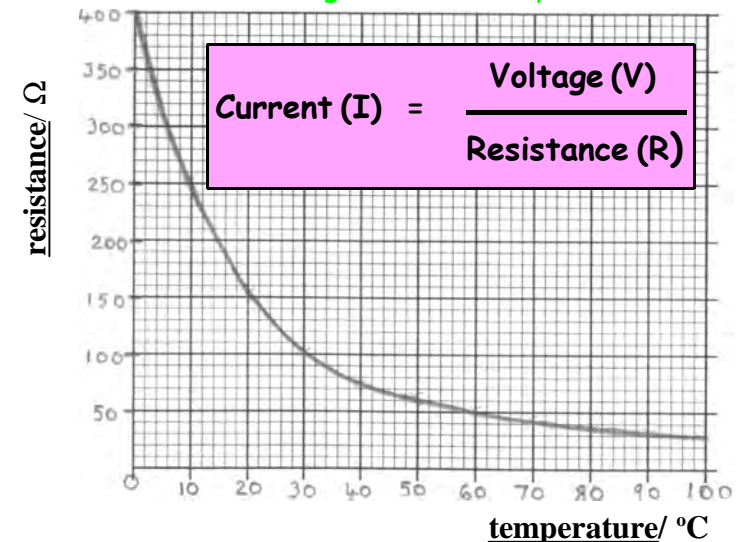This graph shows how the resistance of the thermistor in the above circuit changes as its temperature changes.




Determine the **current** flowing through the circuit when the temperature of the surroundings is:

(a) 10 °C


(b) 30 °C

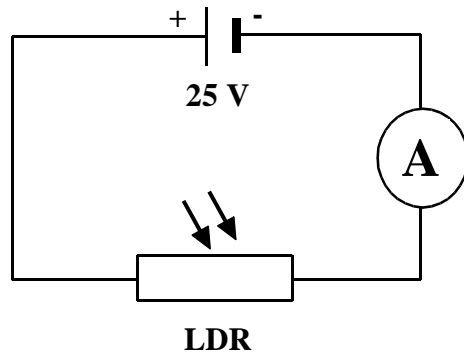(c) 60 °C

The **LDR** in this circuit controls the size of the **current** flowing around the circuit. As the **light level** changes, the **resistance** of the **LDR** changes, so the size of the **current** changes.



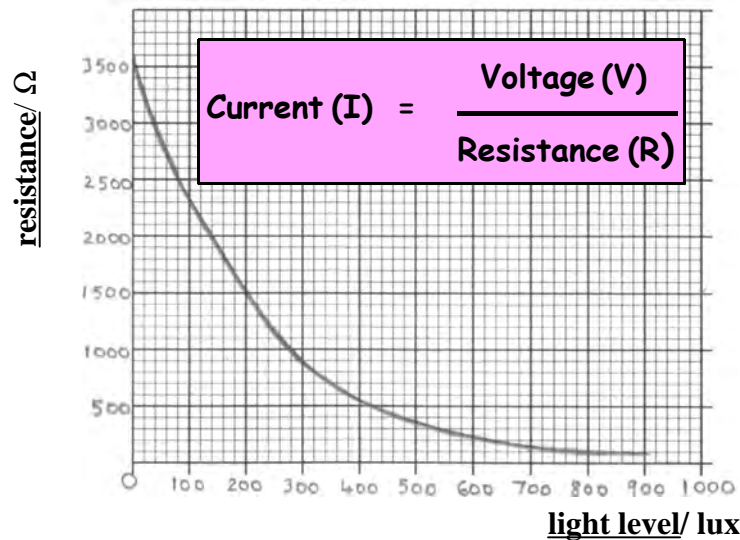This graph shows how the resistance of the LDR in the above circuit changes as the light level changes.



Determine the **current** flowing through the circuit when the light level of the surroundings is:


(a) 100 lux

(b) 400 lux

(c) 800 lux
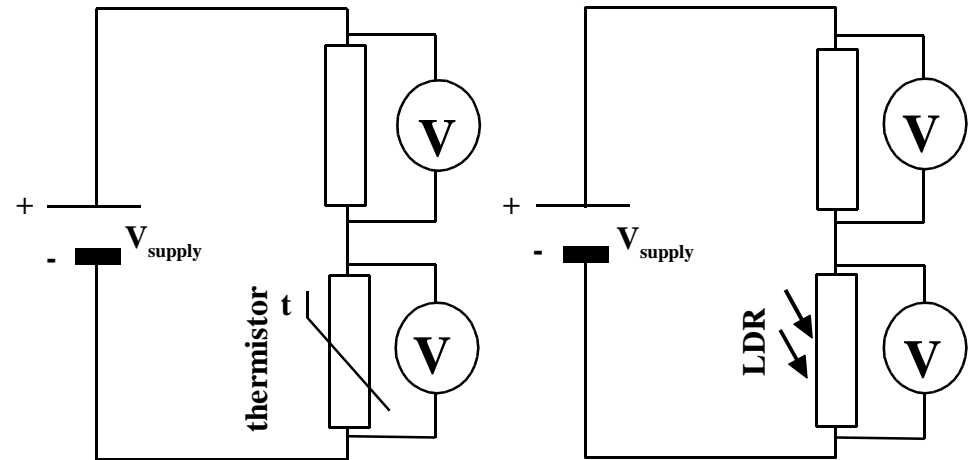
## Voltage Divider Circuits

To obtain a **voltage** from a **thermistor** or **LDR**, we connect them in a **voltage divider** circuit:



As the **resistance** (**R**) of the **thermistor** or **LDR** changes, the **voltage** (**V**) across it changes.

To calculate the **voltage** (**V**) across the **top** or **bottom resistor** in a **voltage divider**, we use the "**voltage divider equation**" :





$$V_{\text{top}} = \frac{R_{\text{top}}}{R_{\text{top}} + R_{\text{bottom}}} \times V_{\text{supply}}$$

or

$$V_{\text{bottom}} = \frac{R_{\text{bottom}}}{R_{\text{top}} + R_{\text{bottom}}} \times V_{\text{supply}}$$

$$\text{voltage across top resistor} + \text{voltage across bottom resistor} = \text{supply voltage}$$

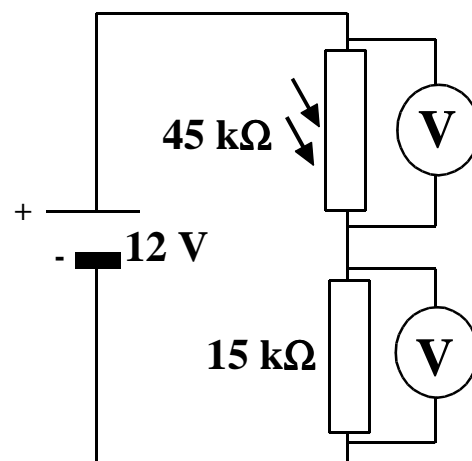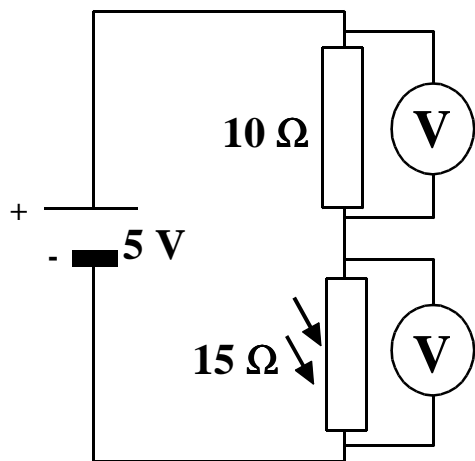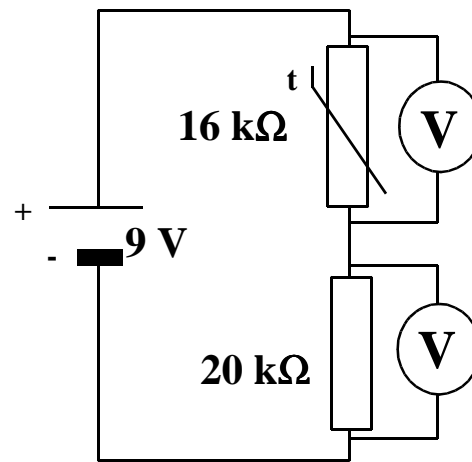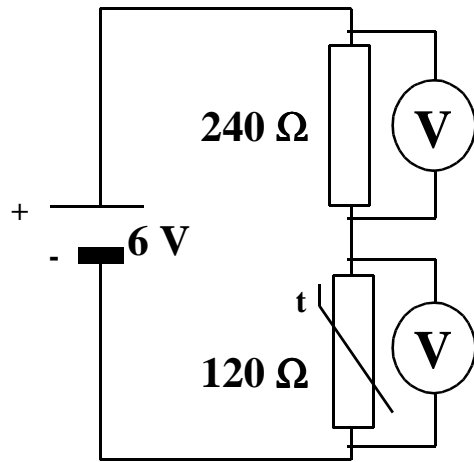For each voltage divider circuit, calculate the voltage across the bottom resistor and the voltage across the top resistor:






In a **voltage divider circuit**, the **voltage** across a resistor is related to its **resistance**.

The **h** \_\_\_\_\_ the **resistance** of a resistor, the **h** \_\_\_\_\_ the **voltage** across it.

This equation applies:
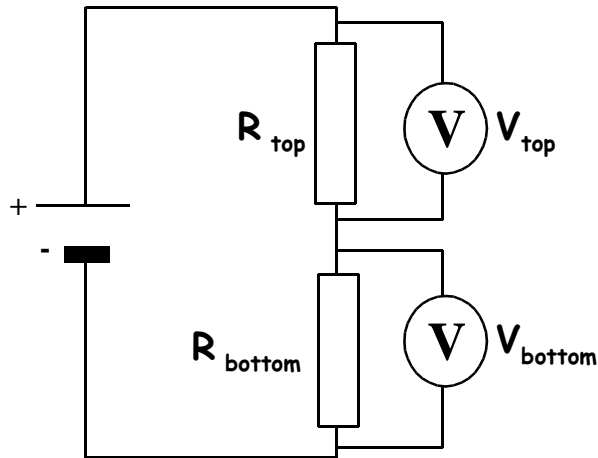
$$\frac{V_{\text{top}}}{V_{\text{bottom}}} = \frac{R_{\text{top}}}{R_{\text{bottom}}}$$







Because a **voltage divider circuit** is a **series circuit**, the **current** passing through both resistors is the **s** \_\_\_\_\_.

$$\text{Current (I)} = \frac{\text{Voltage (V)}}{\text{Resistance (R)}}$$

For each voltage divider circuit below:

(a) Determine the missing quantity:

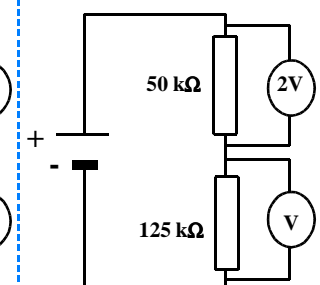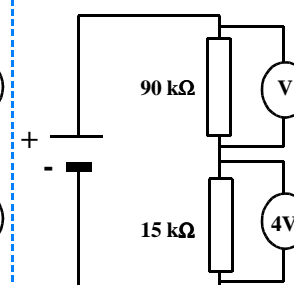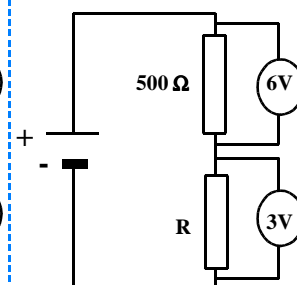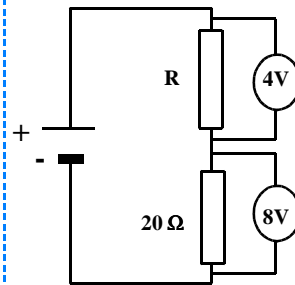(b) Calculate the current passing through both resistors.



Two other **input devices** which can be placed in a **voltage divider circuit** are a **switch** and a **capacitor**:

### switch

When the **switch** is **open**, the **voltmeter** reads \_\_\_\_\_ (which is the \_\_\_\_\_ **voltage**).



The supply voltage splits between the **top resistor** and the **switch** depending on the **resistance** of each.

Because the **open switch** has an **infinitely high** (\_\_\_\_\_) **resistance** compared to the **top resistor**, \_\_\_\_\_ of the **voltage** is found across the **open switch**.

When the **switch** is **closed**, the **voltmeter** reads \_\_\_\_\_.

The **supply voltage** splits between the **top resistor** and the **switch** depending on the **resistance** of each.

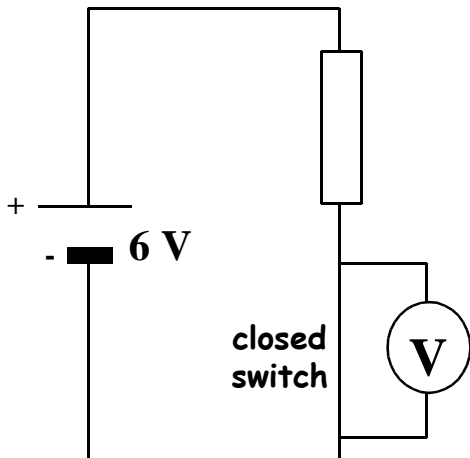
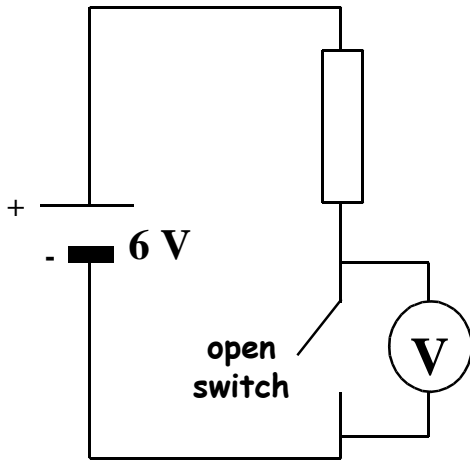
Because the **top resistor** has a much \_\_\_\_\_ **resistance** compared to the **closed switch**, \_\_\_\_\_ of the **voltage** is found across the **top resistor** and \_\_\_\_\_ is found across the **closed switch**.


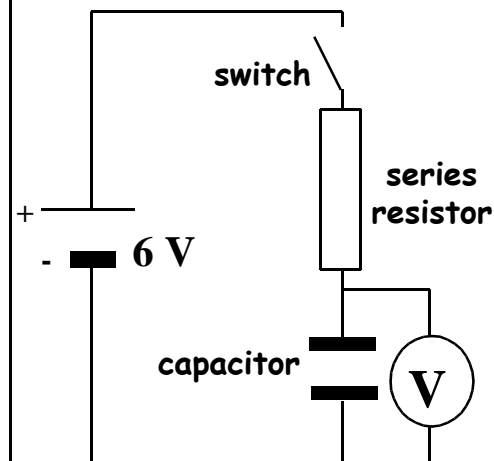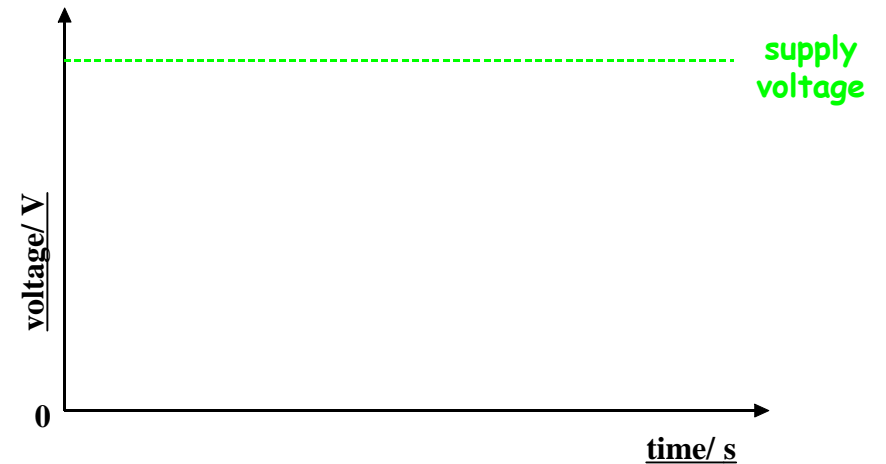
### capacitor

A **capacitor** is a device which stores **electric charge**.

As a **capacitor charges up**, the **voltage across it** increases from \_\_\_\_\_ up to the \_\_\_\_\_ **voltage**:



When the **switch** is **closed**, the **capacitor** starts to **charge up** and the **voltage across it** increases.

The **time** taken for the capacitor to **charge up fully** to the **supply voltage** depends on the **value of the** \_\_\_\_\_ and the value of the **series** \_\_\_\_\_.

By drawing lines, match each input device with the input job it does for a particular electronic system:

- The "singing input" for a karaoke machine.



- The "temperature sensor" for a small electronic thermometer.



- The "light input" for an electronic calculator's power supply.




- The "light detector" for the flash system of a camera.




### Input devices




● microphone

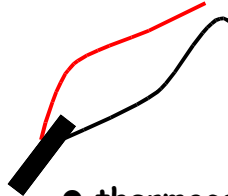


● thermocouple

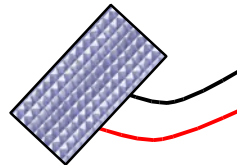


● solar cell

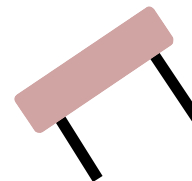


● thermistor

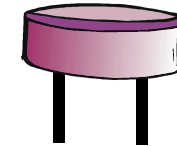


● light dependent resistor (LDR)

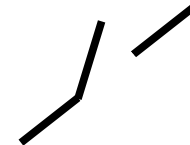


● switch

 


● capacitor

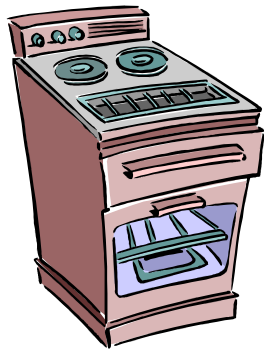

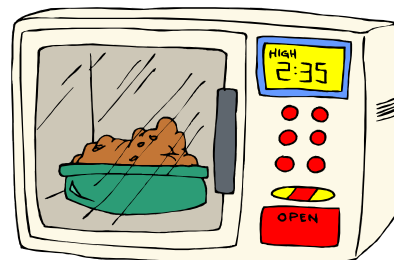- The "temperature sensor" for a very hot electric oven.



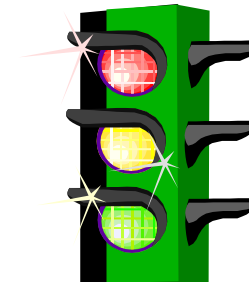- The "on/off input" for a microwave oven.



- The "time delay input" for a pedestrian-controlled crossing. (The red light switches on when someone has pressed the "wish to cross" button and the voltage has built up from zero to a high enough value).

### 3) OUTPUT DEVICES

Output devices take the **electrical signal** (**electrical energy**) from the **process part** of an electronic system and change it into **a useful form of energy**.

For example:

#### • Analogue Output Devices

The output can have many \_\_\_\_\_ values.


Often, the value keeps \_\_\_\_\_.

##### • loudspeaker



\_\_\_\_\_ → \_\_\_\_\_  
The **v** \_\_\_\_\_ and **f** \_\_\_\_\_  
of the sound keep changing.

##### • electric motor

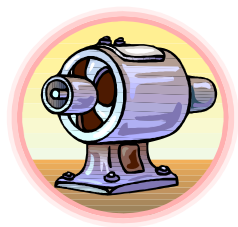

\_\_\_\_\_ → \_\_\_\_\_  
The **s** \_\_\_\_\_ of the turning motor  
can be changed to many different  
values.

##### • moving coil meter



\_\_\_\_\_ → \_\_\_\_\_  
The **p** \_\_\_\_\_ of the pointer on  
the scale can change from anywhere  
between the **far l** \_\_\_\_\_ and **far r** \_\_\_\_\_.


#### • Digital Output Devices

These have only \_\_\_\_\_ values.

We describe these values in different ways:

\_\_\_\_\_/\_\_\_\_/\_\_\_\_ or \_\_\_\_/\_\_\_\_/\_\_\_\_ or \_\_\_\_/\_\_\_\_


##### • solenoid

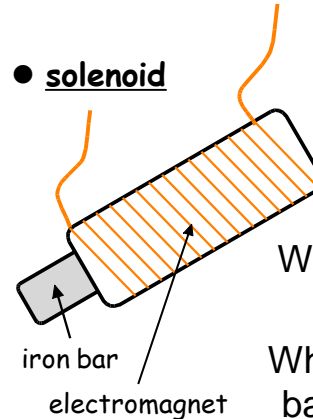

\_\_\_\_\_ → \_\_\_\_\_  
When the solenoid is **ON**, the iron  
bar in the centre is pulled **i** \_\_\_\_\_.

When the solenoid is **OFF**, the iron  
bar in the centre is pushed **o** \_\_\_\_\_.

##### • relay

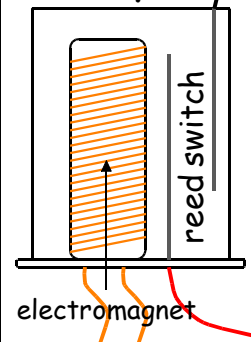


\_\_\_\_\_ → \_\_\_\_\_

When the relay is **ON**, the  
reed switch is **c** \_\_\_\_\_.

When the relay is **OFF**, the  
reed switch is **o** \_\_\_\_\_.

##### • light emitting diode (LED)

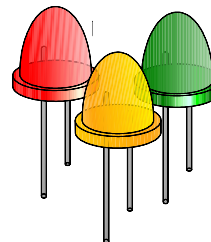


\_\_\_\_\_ → \_\_\_\_\_

The **LED** is either **o** \_\_\_\_\_ or **o** \_\_\_\_\_.

Its **b** \_\_\_\_\_  
does not change.



## Connecting LED's in a Circuit

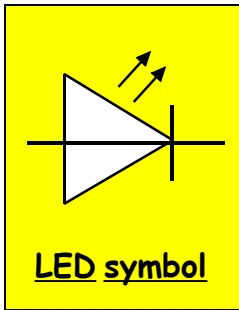

An **LED** will only light if it is connected **one way round**:

Put a **tick** or **cross** in each box below to show the circuit in which the LED will light.

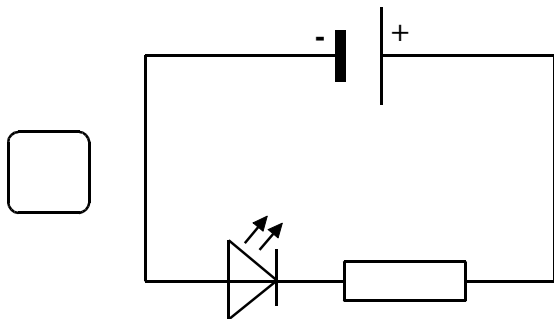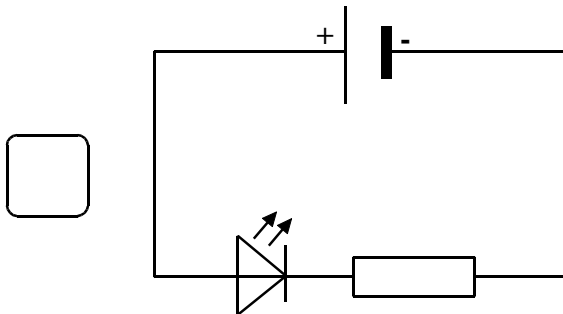For the circuit in which the LED lights, draw **arrows** to show the direction in which electrons flow.




A **r** \_\_\_\_\_ is connected beside (in **s** \_\_\_\_\_ with) the **LED**.

This is needed to \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_
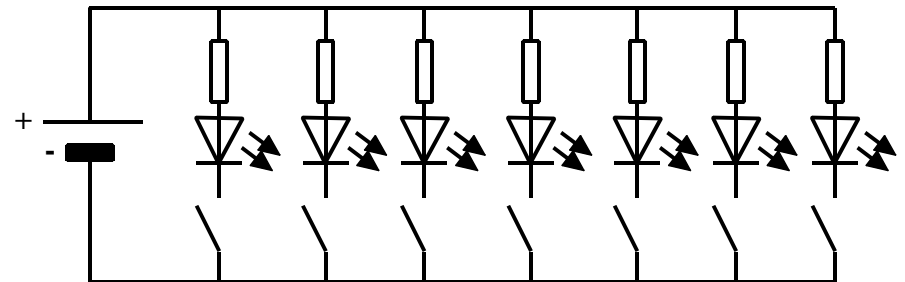
## The Seven-Segment Display



**Seven** separate **LED's** can be arranged to form the shape of a **number** e \_ \_ \_ \_ - This is called a **7- s** \_ \_ \_ \_ \_ **d** \_ \_ \_ \_ \_.

Each **LED** can be switched **on** or **off** s \_ \_ \_ \_ \_ using the electric circuit below:




This allows **any number** from \_ to \_ to be displayed.

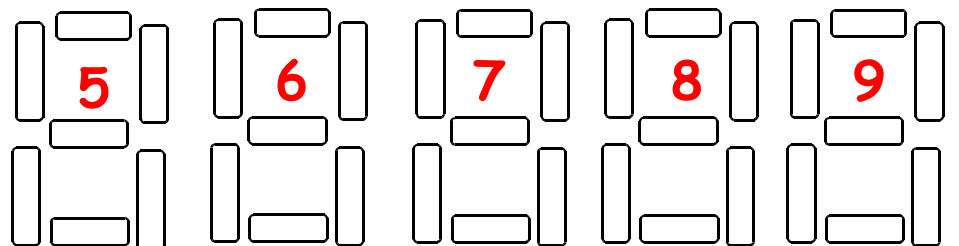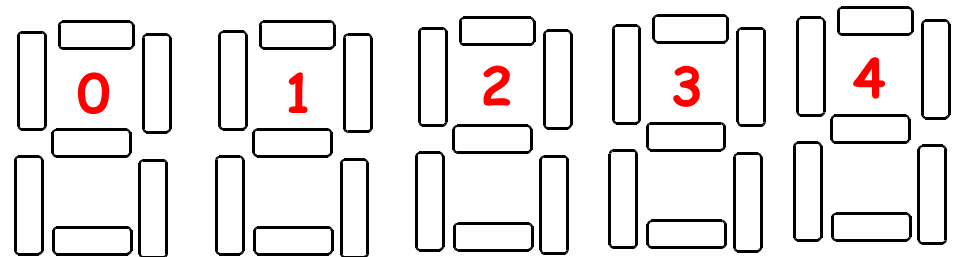Colour in the **LED's** which must be lit to produce these numbers:


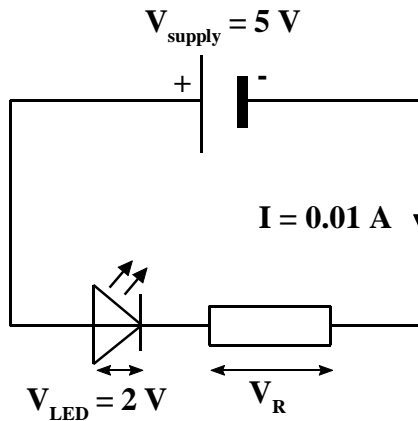
## Calculating the Resistance of the Series Resistor Protecting an LED



For the electric circuit shown below, the maximum voltage the **LED** can safely take is 2 V. The current is 0.01 A.







$$\begin{aligned}\text{Voltage across resistor } (V_R) &= V_{\text{supply}} - V_{\text{LED}} \\ &= 5 \text{ V} - 2 \text{ V} \\ &= 3 \text{ V}\end{aligned}$$

$$\begin{aligned}\text{Resistance of resistor } (R) &= \frac{V_R}{I} \\ &= \frac{3 \text{ V}}{0.01 \text{ A}} = 300 \Omega\end{aligned}$$

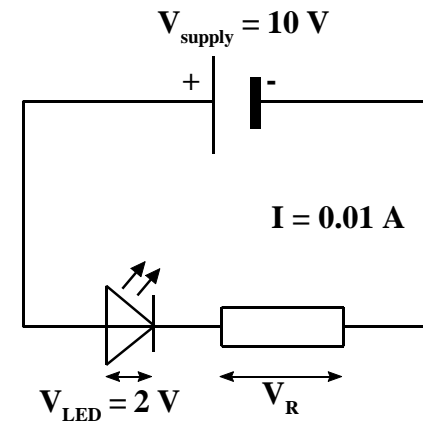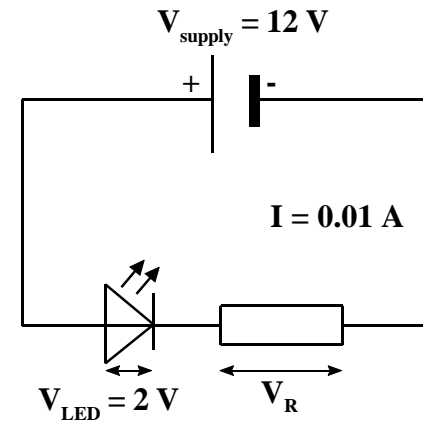Calculate the resistance of the protective resistor in each of the following LED circuits:



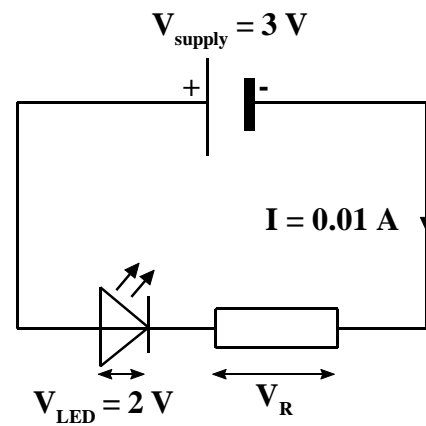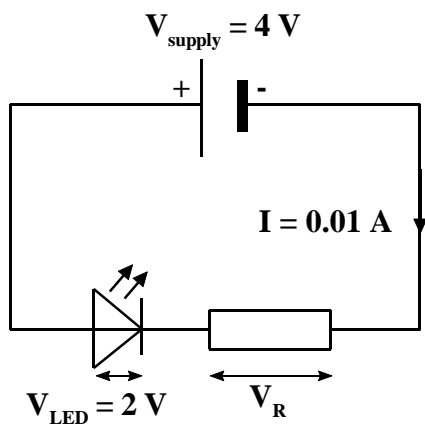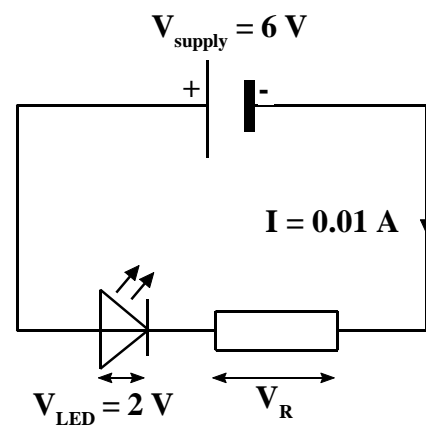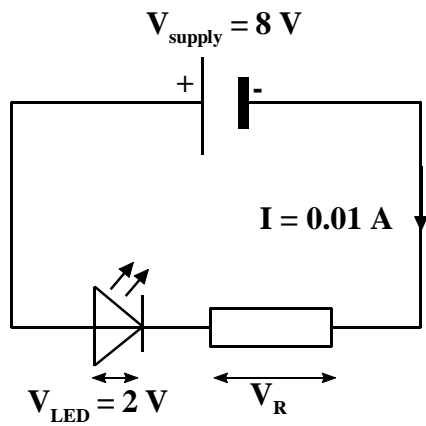

By drawing lines, match each output device with the job it does in 2 different electronic systems:


● loudspeaker




● electric motor




● moving coil meter

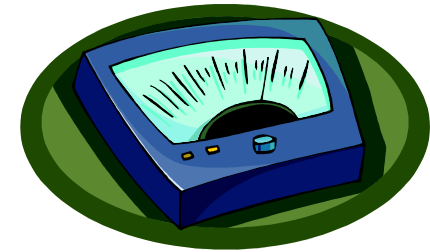

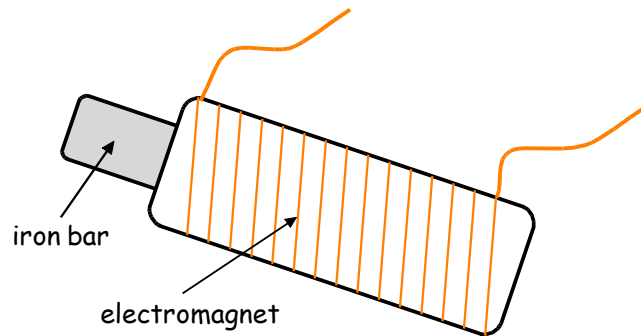
- An electrically-operated door bolt.
- Turning the blades of a fan.
- Switching on a motor.
- Displaying numbers in a seven segment display.
- Turning the chuck of an electric drill.
- Pushing boxes off a conveyor belt.
- Giving out sound from a radio.
- Switching on a device in a nuclear reactor.
- Showing a voltage reading.
- Showing a current reading.
- Showing that a radio is switched on.



● solenoid

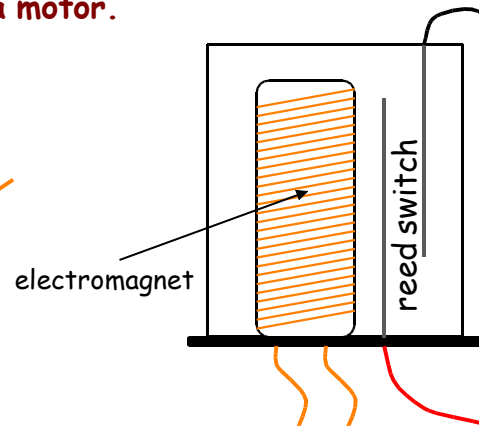

● relay

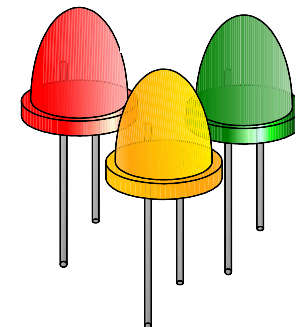

● light emitting diode



## 4) DIGITAL PROCESS DEVICES


**Process devices** take information from **input devices**, **process the information**, then **send it to** an **output device**.

### Logic Gate Circuits


A logic gate **outputs** a signal  
( \_\_\_\_/\_\_\_\_ or \_\_\_\_/\_\_\_\_ or \_\_\_\_/\_\_\_\_ )  
depending on the signal(s) **input** to it.

**Logic gates** may have one or more **inputs**.

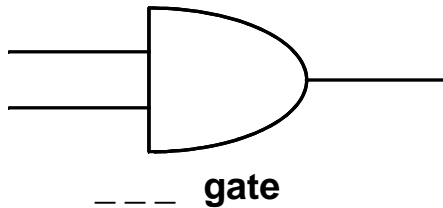
A **t** \_\_\_\_ **t** \_\_\_\_ shows the **output** for all possible  
**input** combinations.



truth table		
INPUT A	INPUT B	OUTPUT C

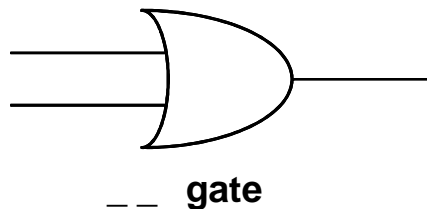


truth table		
INPUT A	INPUT B	OUTPUT C

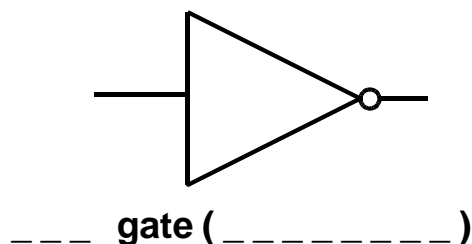


truth table	
INPUT A	OUTPUT B

**Control circuits** in **electronic devices** use a  
**combination of logic gates**.

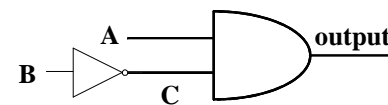
For the **combinations of logic gates** shown, complete  
the **truth tables**:



A	B	C	output
0	0		
0	1		
1	0		
1	1		

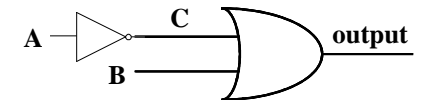


A	B	C	output
0	0		
0	1		
1	0		
1	1		

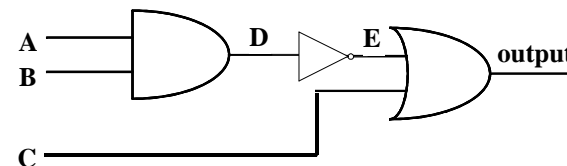


A	B	C	D	E	output
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			


A	B	C	D	E	output
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

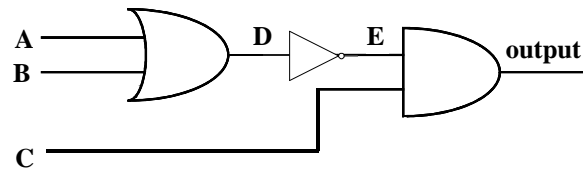

A	B	C	D	E	output
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

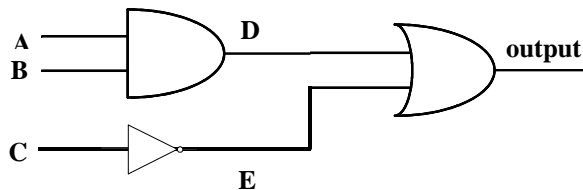


A	B	C	D	E	output
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

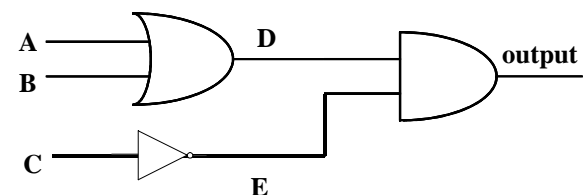
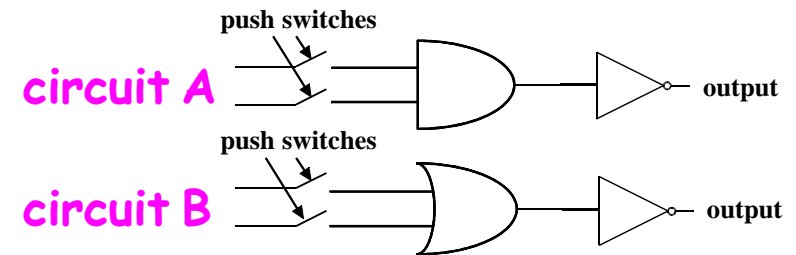
## Simple Logic Gate Control

Two simple logic gate control circuits are shown:



Explain which circuit is used:


By staff in a bank if there is a robbery.

When either of the 2 push switches is closed, the output becomes 0. An electromagnet which holds up a security screen in front of the bank worker is switched off, so the screen falls.




By soldiers preparing to fire a missile.

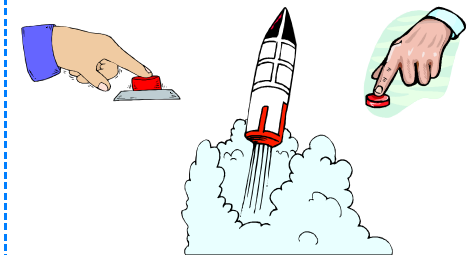When both of the 2 push switches are closed, the output becomes 0 and the safety lock on the firing mechanism is switched off - the missile is launched.



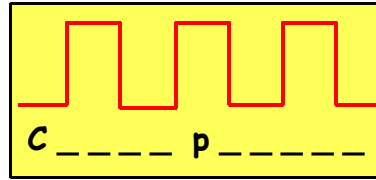
## Clock Pulses

**C** \_\_\_\_\_ **p** \_\_\_\_\_ are a continuous series of **d** \_\_\_\_\_ **p** \_\_\_\_\_ produced at regular time intervals.



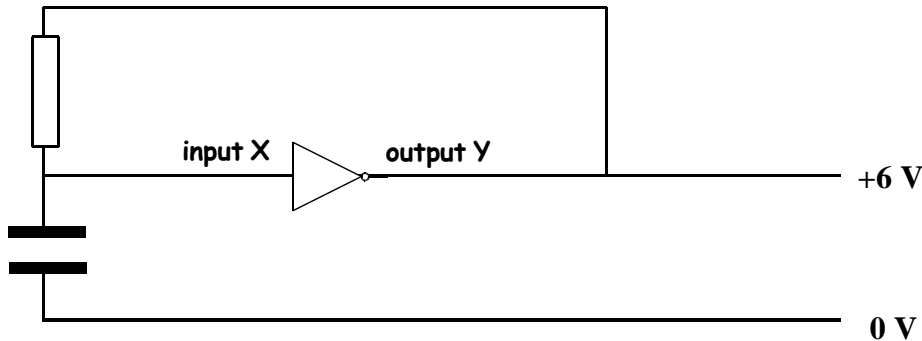They are produced in a **digital circuit** by a **s** \_\_\_\_\_ **o** \_\_\_\_\_ ( **c** \_\_\_\_\_ **p** \_\_\_\_\_ **g** \_\_\_\_\_ ).



1) Capacitor is **uncharged**.

Input X = \_\_ , so output Y = \_\_ .

2) Capacitor **charges up**.


Input X = \_\_ , so output Y = \_\_ .

3) Capacitor **discharges**, so is **uncharged** again.

4) This process keeps **r** \_\_\_\_\_ at **r** \_\_\_\_\_ **i** \_\_\_\_\_ , so produces **c** \_\_\_\_\_ **p** \_\_\_\_\_ .

To get **more clock pulses** every second (increased frequency), we \_\_\_\_\_ the **resistance** of the **resistor** or \_\_\_\_\_ the **capacitance** of the **capacitor** - And vice versa.

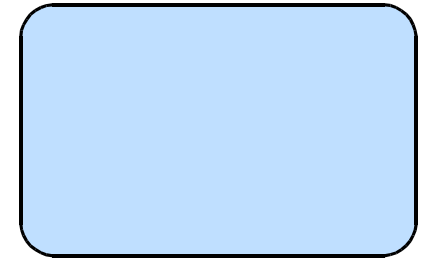(a) On the oscilloscope screen on the right, draw the shape of **clock pulses** output from a **simple oscillator**.



(b) Is a **simple oscillator** circuit analogue or digital?

(c) Sketch a **simple oscillator** circuit. Label the **resistor**, **capacitor** and **inverter**.

(d) Explain how the **simple oscillator** operates.

(e) Describe how to decrease the frequency of the **clock pulses** produced by the **simple oscillator**.




Simple oscillator  
(clock pulse generator)  
circuits produce **digital**  
**clock pulses** for digital  
w \_\_\_\_\_ and  
digital c \_\_\_\_\_.



The **digital clock pulses** are counted by a c \_\_\_\_\_  
circuit - This circuit outputs b \_\_\_\_\_ numbers.

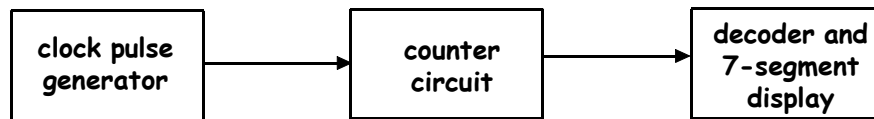The b \_\_\_\_\_ numbers are then fed to a d \_\_\_\_\_  
which changes them to a d \_\_\_\_\_ number for display  
on a 7-s \_\_\_\_\_ d \_\_\_\_\_.



## Changing Binary Numbers to Decimal

**Binary numbers** are used by electronic devices such as  
computers and calculators.

**Binary numbers** are made up of only **ones** and **zeros**  
- For example: **1010**.

This is how to convert a **binary number** into a  
**decimal number**:

$$\begin{array}{cccc}
 1 & 0 & 1 & 0 \\
 \times & \times & \times & \times \\
 8 & 4 & 2 & 1 \\
 \downarrow & \downarrow & \downarrow & \downarrow \\
 8 & + & 0 & + & 2 & + & 0 & = & 10
 \end{array}$$

Convert these **binary numbers** into **decimal numbers**:

1001

0101

0010

0111

0100

0110


0011

1000

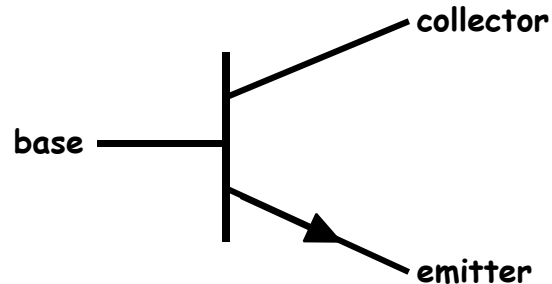
## The Transistor as an Electronic Switch

A **transistor** can be used in a circuit as an **electronic s \_ \_ \_ \_**.

The **circuit symbol** for an **NPN transistor** is shown:



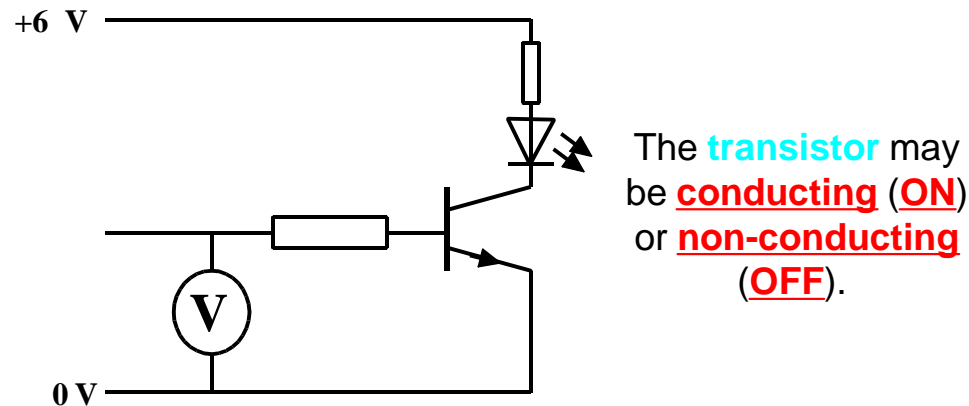A **transistor switching circuit** is shown:




When a **h \_ \_ voltage** (**\_\_\_ V or more**) is applied across the voltmeter, the **transistor** is switched **\_\_\_**.

The **transistor** then switches the **LED** **\_\_\_**.

When a **l \_ \_ voltage** (**less than \_\_\_ V**) is applied across the voltmeter, the **transistor** is switched **\_\_\_**.

The **transistor** then switches the **LED** **\_\_\_**.

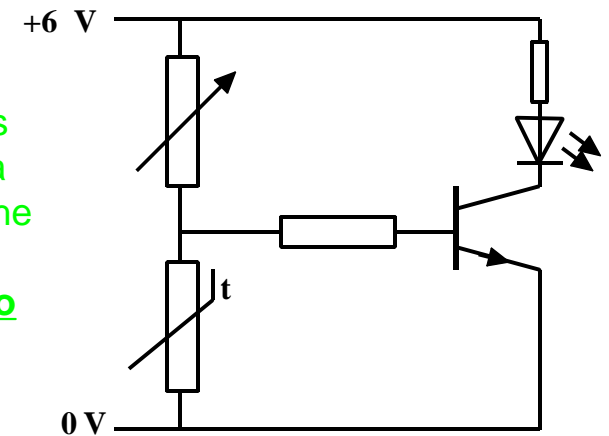
This **transistor switching circuit** is used to switch **on** a warning **LED** when the **temperature** in a greenhouse gets **too low**. Explain how it works:




Redraw the circuit with the **variable resistor** and **thermistor** swapped about. Explain what happens this time when the **temperature falls**.

What is the purpose of the **variable resistor**?

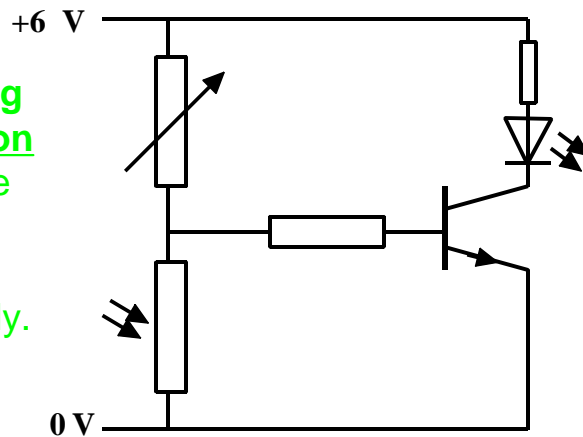This **transistor switching circuit** is used to switch on a warning **LED** when the **light level** in a school library gets too low for people to read comfortably. Explain how it works:



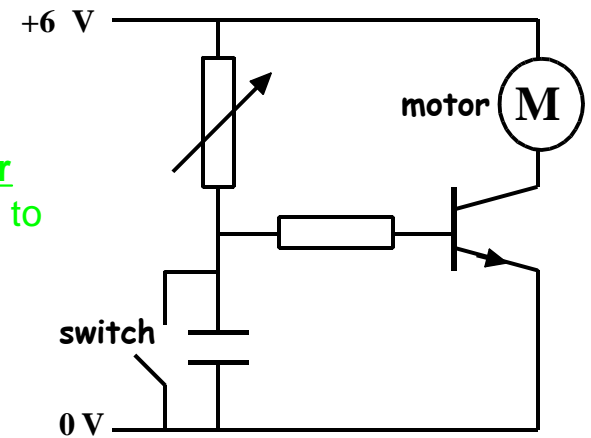This **transistor switching circuit** contains a capacitor and switch. It is used to delay the **motor** switching on.



**WHEN SWITCH S IS OPEN, THE MOTOR IS ON.** Explain what happens when the **switch** is closed:

Redraw the circuit with the **variable resistor** and **LDR** swapped about. Explain what happens this time when the **light level** falls.

Explain what happens when the **switch** is opened again:

What is the purpose of the **variable resistor**?

What is the purpose of the **variable resistor**?


## 5) ANALOGUE PROCESS DEVICES-AMPLIFIERS

**Amplifiers** play an important part in electronic devices which have a **loudspeaker output** - For example:

The **amplifier** increases the **a** \_\_\_\_\_ of the electrical **i** \_\_\_\_\_ **signal**.


As a result, the **o** \_\_\_\_\_ **signal** has a greater **amplitude** than the **input signal** - It now has enough **e** \_\_\_\_\_ to power the **loudspeaker**.

For example, a karaoke machine:

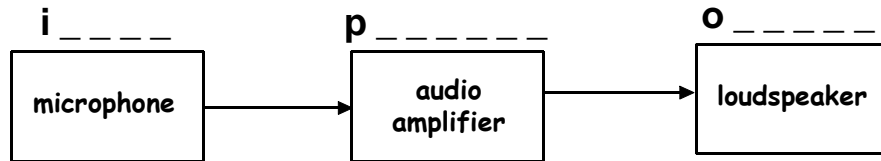

The **audio amplifier** does not change the **f** \_\_\_\_\_ of the **input signal** - If the **input signal** has a **frequency** of **1 000 Hz**, the **output signal** has a **frequency** of \_\_\_\_\_ **Hz**.

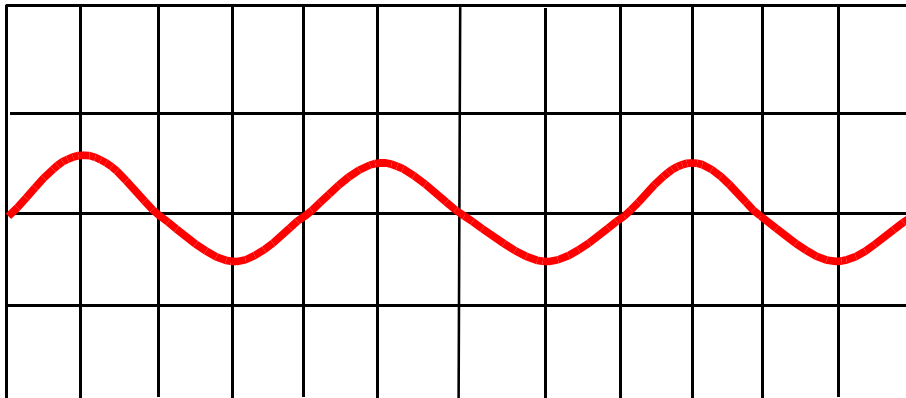The trace below shows the **electrical signal** from a **microphone** which is being input to an **amplifier**. On the same trace, draw the **possible shape** of the **output signal**.



## Voltage Gain of an Amplifier

In an **electronic system**, the **electrical signals** are usually **voltages**. The number of times an **amplifier** increases the **amplitude** of an **input voltage** by is known as the **v** \_\_\_\_\_ **g** \_\_\_\_\_ of the **amplifier** - This does not have a **u** \_\_\_\_\_.

$$\text{voltage gain} = \frac{\text{output voltage}}{\text{input voltage}}$$

In each case below, calculate the **voltage gain** of the **amplifier**:

input voltage = 12 V,  
output voltage = 36 V

input voltage = 2.5 V,  
output voltage = 75 V

input voltage = 1.2 V,  
output voltage = 24 V

input voltage = 0.15 V,  
output voltage = 45 V

input voltage = 0.25 mV,  
output voltage = 12.5 mV

input voltage = 100 mV,  
output voltage = 2 000 mV

In each case below, calculate the **output voltage** from the **amplifier**:

input voltage = 0.15 V,  
voltage gain of amplifier = 200

input voltage = 0.15 V,  
voltage gain of amplifier = 80

input voltage = 18 mV,  
voltage gain of amplifier = 30

input voltage = 12.5 mV,  
voltage gain of amplifier = 20

In each case below, calculate the **input voltage** to the **amplifier**:


voltage gain of amplifier = 250,  
output voltage = 90 V

voltage gain of amplifier = 15,  
output voltage = 25.5 V

voltage gain of amplifier = 120,  
output voltage = 36 mV

voltage gain of amplifier = 75,  
output voltage = 210 mV
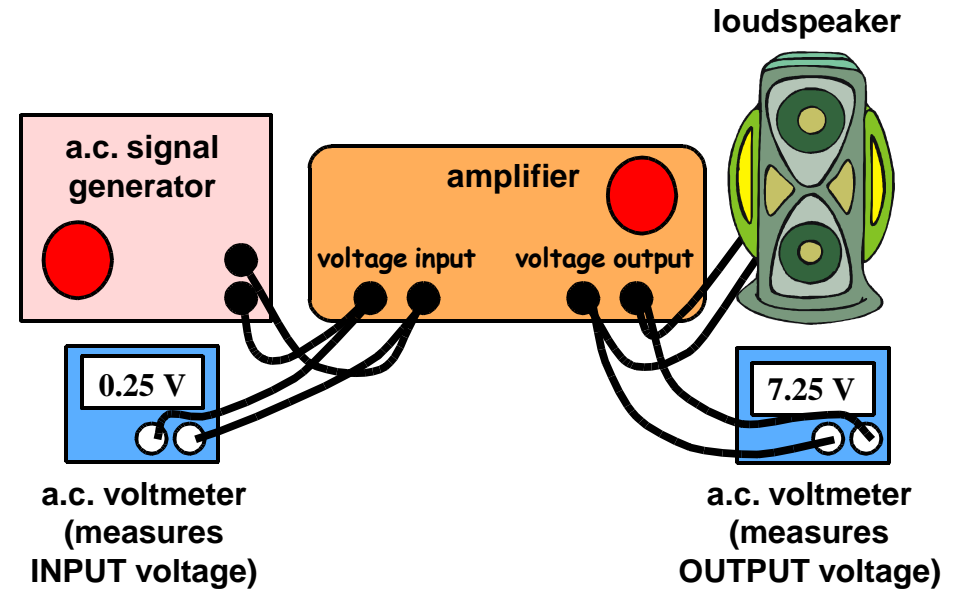
## Experiment to Measure the Voltage Gain of an Amplifier



Describe how you would use this apparatus to measure the **voltage gain** of the amplifier.



## Amplifier Power

The electrical **power input** to and **power output** from an **amplifier** can be calculated using the formula:

$$\text{power} = \frac{\text{voltage}^2}{\text{resistance}}$$

Note - In amplifier problems, the word "impedance" is sometimes used instead of the word "resistance".

In each case, calculate the **power input** or **power output** of the amplifier:

input voltage = 12 V,  
resistance = 6  $\Omega$

output voltage = 12 V,  
resistance = 3  $\Omega$

input voltage = 6 V,  
resistance = 9  $\Omega$

output voltage = 2 V,  
resistance = 8  $\Omega$

input voltage = 5 V,  
resistance = 2.5  $\Omega$

output voltage = 9 V,  
resistance = 18  $\Omega$

input voltage = 8 V,  
resistance = 8  $\Omega$

output voltage = 100 V,  
resistance = 25  $\Omega$

input voltage = 2.5 V,  
resistance = 6.25  $\Omega$

output voltage = 5.5 V,  
resistance = 1.25  $\Omega$

input voltage = 13 V,  
resistance = 26  $\Omega$

output voltage = 100 V,  
resistance = 500  $\Omega$

input voltage = 5.5 V,  
resistance = 0.25  $\Omega$

output voltage = 7.5 V,  
resistance = 1.25  $\Omega$

## Power Gain of an Amplifier

The number of times an **amplifier** increases the **amplitude** of an **input power** by is known as the

**p** \_ \_ \_ **g** \_ \_ \_ of the **amplifier**

- This does not have a **u** \_ \_ \_.

$$\text{power gain} = \frac{\text{output power}}{\text{input power}}$$

In each case below, calculate the **power gain** of the **amplifier** which has **amplified** the **input power**:

input power = 10 W,  
output power = 300 W

input power = 3 W,  
output power = 180 W

input power = 2.5 W,  
output power = 15 W

input power = 0.15 W,  
output power = 36 W

input power = 0.25 mW,  
output power = 525 mW

input power = 10mW,  
output power = 350 mW

A loudspeaker of resistance  $8\ \Omega$  has 6 volts across it.

- (a) Calculate the **power output** of the loudspeaker.
- (b) Find the **power gain** of the amplifier to which the loudspeaker is connected if the input power to the amplifier is 0.05 W.

- 
- (a) Calculate the **power output** of a loudspeaker of resistance  $12\ \Omega$  which has 24 V across it.
  - (b) Find the **power gain** of the amplifier to which the loudspeaker is connected if the input power to the amplifier is 0.02 W.

- 
- (a) Calculate the **power output** of a loudspeaker of resistance  $24\ \Omega$  which has 8 V across it.
  - (b) Find the **power gain** of the amplifier to which the loudspeaker is connected if the input power to the amplifier is 0.12 W.